EE 414 Introduction to Analog Integrated Circuits Supplementary Problems

Problem 1: Figure 1 shows a two stage CMOS opamp, calculate:

- a. Slew rate (V/sec.)
- b. Positive and negative output voltage limits (all transistors remain in saturation)
- c. Positive and negative input common voltage limits (all transistors remain in saturation and use nominal parameter values).
- d. Small signal voltage gain (V/V).
- e. Gain-Bandwidth (MHz).
- f. Power dissipation (mW). (Include the 50µA current sink)

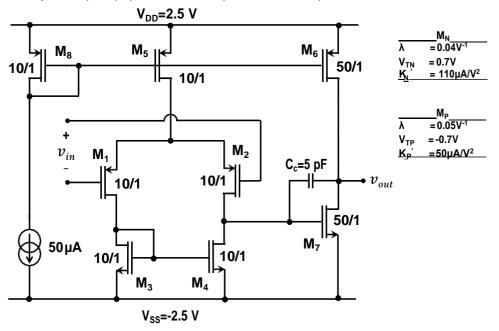


Figure 1

Problem 2: A push-pull output stage is presented in Figure 2.

- a. Find the dc value of the collector currents when $V_{out} = 0$.
- b. What is the maximum and minimum peak output voltage of this amplifier for $R_L=1 \text{ k}\Omega$? What is the maximum output current that can be delivered to the $1 \text{ k}\Omega$ resistive load?
- c. What is the maximum average load power? What is the average power drawn from the sources? What is the efficiency of the circuit?

BJT parameters:

 I_{S1} = 1.11 fA, β_{npn} = β_{pnp} = 100, $V_{BE\ (ON)}$ = 0.6 V, $V_{CE\ (sat)}$ = 0.2 V, V_{CC} = 10 V, V_{T} = 26 mV.

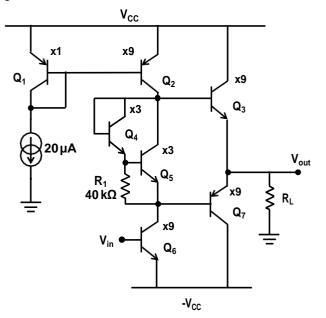


Figure 2