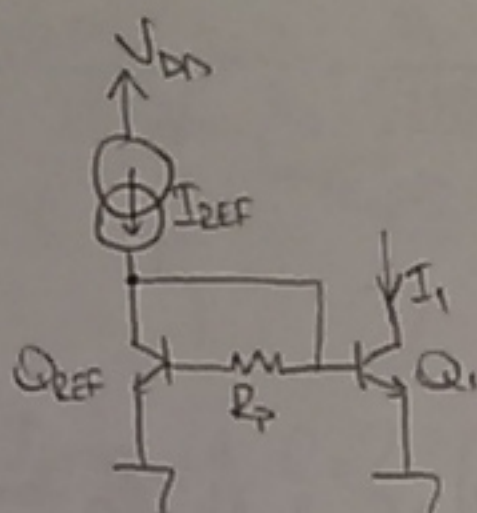



1)



manufacturing error.
 $I_1 \rightarrow 1.1 \times I_1$
 $R_p = 0 \rightarrow R_p = R_p$
 $Q_{REF} \& Q_1$ identical
 $R_p = ?$


Let me first find $I_1 - I_{REF}$ relationship without R_p ;

$Q_{REF} - Q_1$ matched;

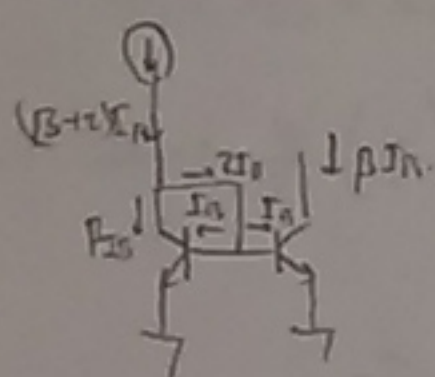

$$\frac{I_1}{I_{REF}} = \frac{\beta I_0}{(\beta+2) I_0} \rightarrow I_1 = \frac{\beta}{\beta+2} I_{REF}$$

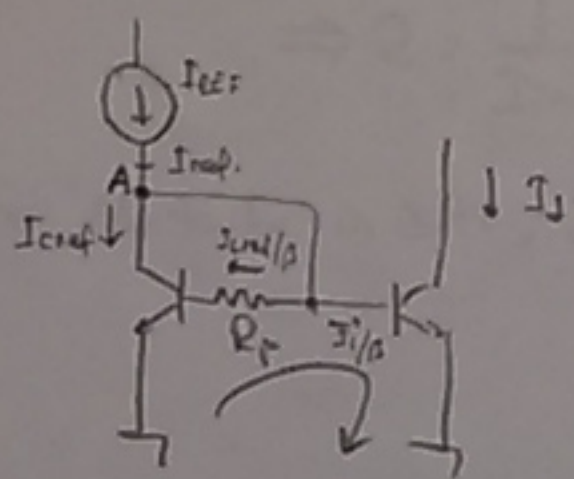In our case, then; $I_1 = 1.1 \cdot \frac{\beta}{\beta+2} \cdot I_{REF}$ (1)



at Loop; $V_{BE,ref} + V_{RP} = V_{BE1}$

$$V_{RP} = \frac{I_{C,ref}}{\beta} R_p = V_{BE1} - V_{BE,ref} = V_T \ln \frac{I_1}{I_{C,ref}}$$

$$R_p = \frac{\beta}{I_{C,ref}} V_T \ln \frac{I_1}{I_{C,ref}} \quad (2)$$

at node A; $I_{C,ref} + \frac{I_{C,ref}}{\beta} + \frac{I_1}{\beta} = I_{REF}$

$$I_{C,ref} = \frac{I_{REF} - \frac{I_1}{\beta}}{1 + \frac{1}{\beta}} \quad (3)$$

Now, plugging (1) into (3).;

$$I_{cref} = \frac{I_{ref} \left(1 - \frac{1.1}{\beta+2}\right)}{\left(1 - \frac{1}{\beta}\right)} = I_{ref} \frac{(\beta+2-1.1)}{\beta+2} \frac{\beta}{\beta+1} = I_{ref} \cdot \frac{(\beta+0.9)\beta}{(\beta+2)(\beta+1)} \quad (4)$$

Put (4), (1) into (2);


$$R_p = \frac{\beta}{I_{SREF}} \cdot V_T \ln \frac{I_1}{I_{C,ref}} = \frac{\beta (\beta+2)(\beta+1)}{I_{ref} (\beta+0.9)\beta} \cdot V_T \ln \left(\frac{(1.1) \frac{\beta}{\beta+2} I_{ref}}{\frac{\beta}{\beta+2} \cdot \frac{\beta+0.9}{\beta+1} I_{ref}} \right)$$

$$R_p = \frac{(\beta+1)(\beta+2)}{(\beta+0.9)} \frac{V_T}{I_{REF}} \cdot \ln \left[\frac{1.1 (\beta+1)}{(\beta+0.9)} \right]$$

$$\text{Let } \alpha = \frac{\beta+1}{\beta+0.9}$$

$$R_p = \alpha (\beta+2) \frac{V_T}{I_{REF}} \cdot \ln [1.1 \alpha]$$

2)

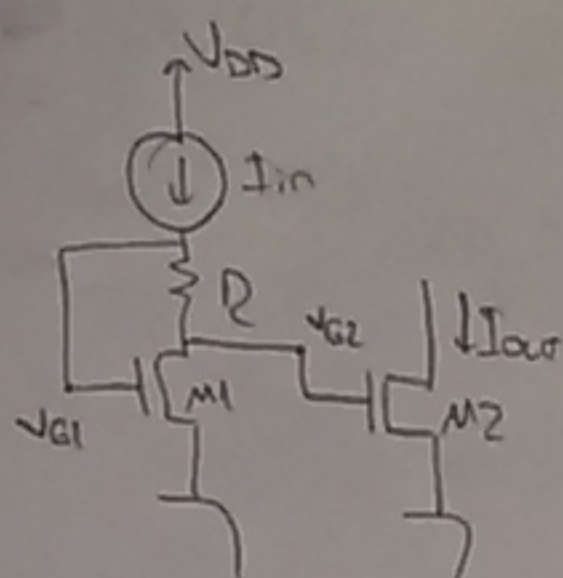

$$I_{out} = 0.1 \mu A$$

$$M_1 \text{ \& } M_2 \text{ are identical} \rightarrow \left(\frac{W}{L}\right)_{M1} = \left(\frac{W}{L}\right)_{M2} = \left(\frac{W}{L}\right)$$

$$k' = 200 \mu A/V^2$$

$$V_{th} = 0.5V$$

a) $I_m = 1 \mu A$, $R = ?$, $\left(\frac{W}{L}\right) = ?$

$$I_{out} = \frac{k'}{2} \left(\frac{W}{L}\right) (V_{G2} - V_T)^2, \quad V_{G2} = V_{D1}$$

$$I_m = \frac{k'}{2} \left(\frac{W}{L}\right) (V_{G1} - V_T)^2 \rightarrow V_{G1} = \sqrt{\frac{2I_m}{k'(\frac{W}{L})}} + V_T$$

$$V_{G1} = V_{G2} + RI_m \rightarrow V_{G2} = V_{G1} - RI_m$$

$$I_{out} = \frac{k'}{2} \left(\frac{W}{L}\right) (V_{G1} - RI_m - V_T)^2 = \frac{k'}{2} \left(\frac{W}{L}\right) \left(\sqrt{\frac{2I_m}{k'(\frac{W}{L})}} - RI_m\right)^2$$

$$-I_m R = \sqrt{\frac{2I_{out}}{k'(\frac{W}{L})}} - \sqrt{\frac{2I_m}{k'(\frac{W}{L})}}$$

$$\Rightarrow R = \frac{1}{I_m} \left(\sqrt{\frac{2I_m}{k'(\frac{W}{L})}} - \sqrt{\frac{2I_{out}}{k'(\frac{W}{L})}} \right) \quad (1)$$

For M_1 to be in SAT; $V_{G1} - V_{th} > 2nV_T \rightarrow$ for strong inversion to be satisfied.

$$\sqrt{\frac{2I_m}{k'(\frac{W}{L})}} > 78mV$$

$$\left(\frac{W}{L}\right) < 1643$$

according to Gray & Meyer's book: $0 \leq V_{GS} - V_T < 2nV_T$ moderate inversion
 $V_{GS} - V_{th} > 2nV_T$ strong inv.

from page 300 of Gray & Meyer for strong inversion condition $V_G - V_{th} > 78mV = 3kT/q$
 "nondegenerate"

$$\bullet V_{D1} > V_{G1} - V_{th}$$

$$V_{G2} - V_{G1} > -V_{th}$$

$$V_{G1} - RI_m - V_{G1} > -V_{th}$$

$$RI_m < V_{th} \quad (2)$$

put (1) into (2);

$$R I_m < V_{th} \rightarrow \sqrt{\frac{2 I_m}{k' (\frac{W}{L})}} - \sqrt{\frac{2 I_{out}}{k' (\frac{W}{L})}} < 0.5$$

$$\sqrt{\frac{2 \cdot 1}{200 (\frac{W}{L})}} - \sqrt{\frac{2 (0.1)}{200 (\frac{W}{L})}} < 0.5$$

$$\sqrt{(\frac{W}{L})^{-1}} (0.1 - 0.032) < 0.5$$

$$\frac{W}{L} > 0.0187$$

$$1.6437 > \frac{W}{L} > 0.0187$$

$$R = \frac{1}{I_m} \left(\sqrt{\frac{2 I_m}{k' (\frac{W}{L})}} - \sqrt{\frac{2 I_{out}}{k' (\frac{W}{L})}} \right) \quad \text{putting limiting } \frac{W}{L} \text{ values to this expression}$$

$$53.33 \text{ k}\Omega < R < 500 \text{ k}\Omega$$

b - $R = 10\text{ k}\Omega$, $I_{in} = ?$

2 SAT conditions;

- $V_{G1} - V_{th} > 78\text{ mV}$

$$\sqrt{\frac{2I_{in}}{k'(\frac{W}{L})}} > 78\text{ mV} \quad (b1)$$

- $RI_{in} < V_{th} \quad (b2)$

and from (1) $RI_{in} = \left(\sqrt{\frac{2I_{in}}{k'(\frac{W}{L})}} - \sqrt{\frac{2I_{out}}{k'(\frac{W}{L})}} \right) \quad (b3)$

Solving (b1) & (b3) simultaneously gives $(\frac{W}{L})$'s upper limit:

From (b1) at boundary: $\sqrt{\frac{I_{in}}{(\frac{W}{L})}} = 7.8 \times 10^{-4} \rightarrow$ put this into (b3)

$$10000(7.8 \times 10^{-4})^2 \left(\frac{W}{L} \right) = 0.078 - 0.0316 \sqrt{\frac{1}{(\frac{W}{L})}}$$

$$\Rightarrow \text{lower limit for } \left(\frac{W}{L} \right) = 0.1685. \quad \left(\text{I utilized Wolfram Alpha for this solution.} \right)$$

Corresponding $I_{in} = 0.102 \mu\text{A}$

For the other condition (b2):

$$I_{in} < \frac{V_{th}}{R} = \frac{0.5}{10000} = 50 \mu\text{A} \rightarrow \text{put into (b3)}$$

$$0.5 = \left(\sqrt{\frac{2 \cdot 50}{200 \left(\frac{W}{L} \right)}} - \sqrt{\frac{2 \cdot (0.1)}{200 \left(\frac{W}{L} \right)}} \right) = \sqrt{\frac{1}{\frac{W}{L}}} \left(\sqrt{0.5} - \sqrt{1/1000} \right)$$

$$\frac{W}{L} = 1.162$$

$$0.1685 < \left(\frac{W}{L} \right) < 1.162$$

$$0.102 \mu\text{A} < (I_{in}) < 50 \mu\text{A}$$


3) no body effect

$$A=100, R_{in}=\infty, V_o = A(V_+ - V_-) \rightarrow \text{ac analysis}$$


$$V_+ = V_- \rightarrow \text{DC analysis}$$

$$M_{1-4}: \frac{W}{L}, M_5 \rightarrow \left(\frac{W}{L}\right) = ? \text{ to min the gain error.}$$

$$\text{Gain error? } R_{out} = ?$$

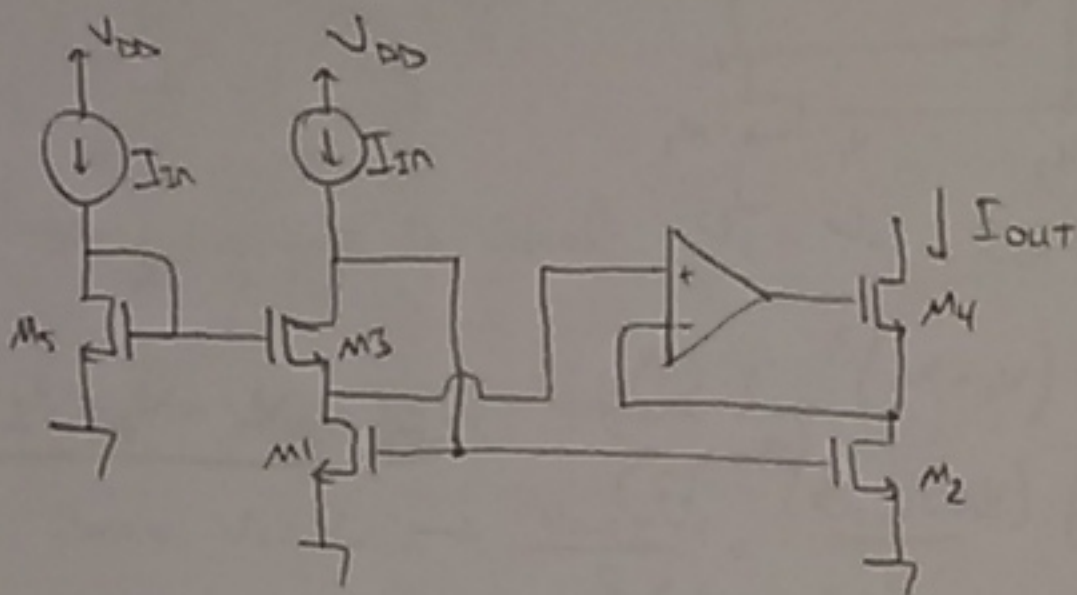


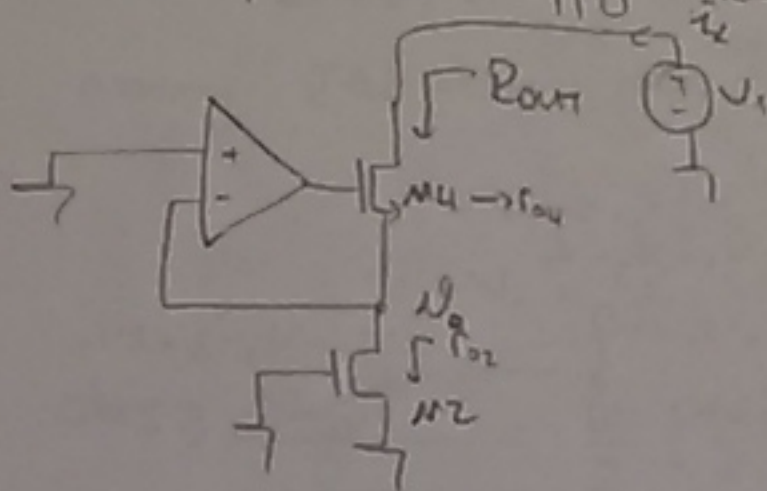$R_{out} \rightarrow$ kill input sources; apply a test source to output;



$$V_a = i_x r_{o2}$$
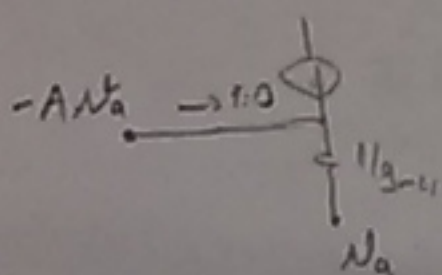
$$i_x = \frac{V_x - V_a}{r_{o4}} + g_{m4} (-A V_a - V_a)$$




$$i_x = \frac{V_x - i_x r_{o2}}{r_{o4}} + g_{m4} (-A i_x r_{o2} - i_x r_{o2})$$

$$i_x (r_{o4} + r_{o2} + g_{m4} r_{o4} (A r_{o2} + r_{o2})) = V_x$$

$$\boxed{\frac{V_x}{i_x} = R_{out} = r_{o4} + r_{o2} + g_m r_{o4} r_{o2} (A+1)}$$

$\Rightarrow R_{out}$ is further increased by the factor $(A+1)$

Consider DC voltages;

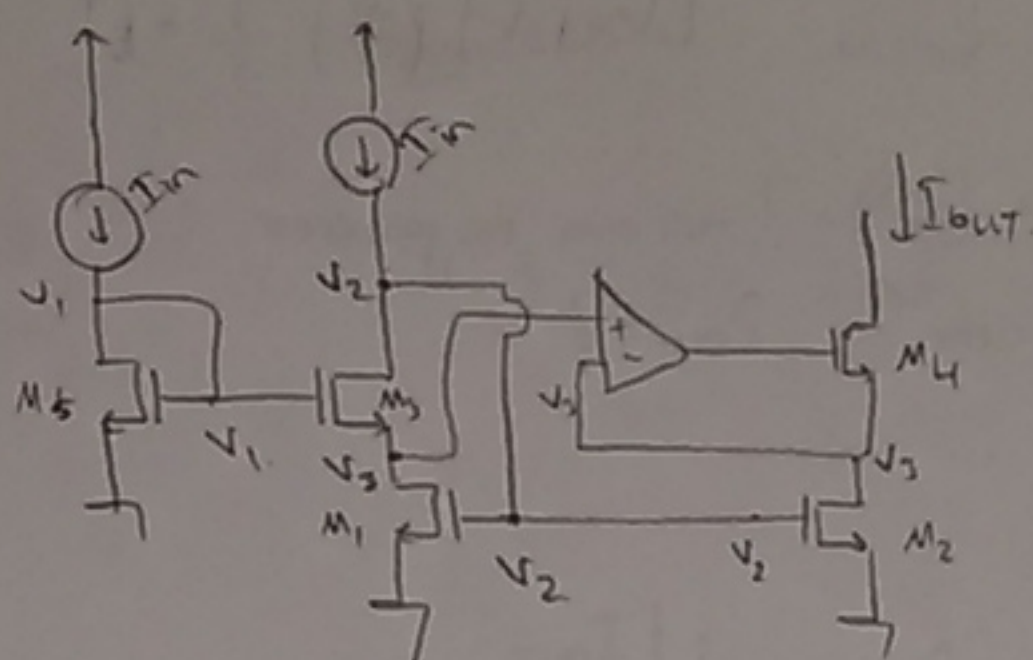

$$M_5 \rightarrow I_{in} = \frac{k}{2} \left(\frac{W}{L} \right)_5 (V_1 - V_T)^2 \quad (1)$$

$$M_3 \rightarrow I_{in} = \frac{k}{2} \left(\frac{W}{L} \right) (V_1 - V_3 - V_T)^2 \quad (2)$$

$$M_1 \rightarrow I_{in} = \frac{k}{2} \left(\frac{W}{L} \right) (V_2 - V_T)^2 \quad (3)$$

$$\Rightarrow \underline{V_1 = V_2 + V_3}$$

for both M_1 & M_3 to be open and in SAT.

$$\begin{aligned} & \left. \begin{aligned} V_1 &> V_T \\ V_2 &> V_T \end{aligned} \right\} \begin{aligned} & V_3 > V_2 - V_T \\ & V_2 - V_3 > V_1 - V_3 - V_T \end{aligned} \\ & \left\{ \begin{aligned} V_3 - V_2 &> -V_T \\ V_2 - V_1 &> -V_T \end{aligned} \right\} \rightarrow \begin{aligned} & V_3 - V_1 > -2V_T \\ & V_1 - V_3 < 2V_T \end{aligned}$$


So the stable solution with systematic error \Rightarrow
(all V_{DS} are equal)

$$\begin{aligned} V_3 &= V_T \\ V_2 &= 2V_T \\ V_1 &= 3V_T \end{aligned}$$

Thus, $\left(\frac{W}{L} \right)_5 = \frac{1}{4} \left(\frac{W}{L} \right)$ from current equations (1) & (2).

Having chosen $\left(\frac{W}{L} \right)_5 = \frac{1}{4} \left(\frac{W}{L} \right)$ the systematic error is zero, '0'.
 $V_{DS1} = V_{DS3} = V_{DS5}$

4)

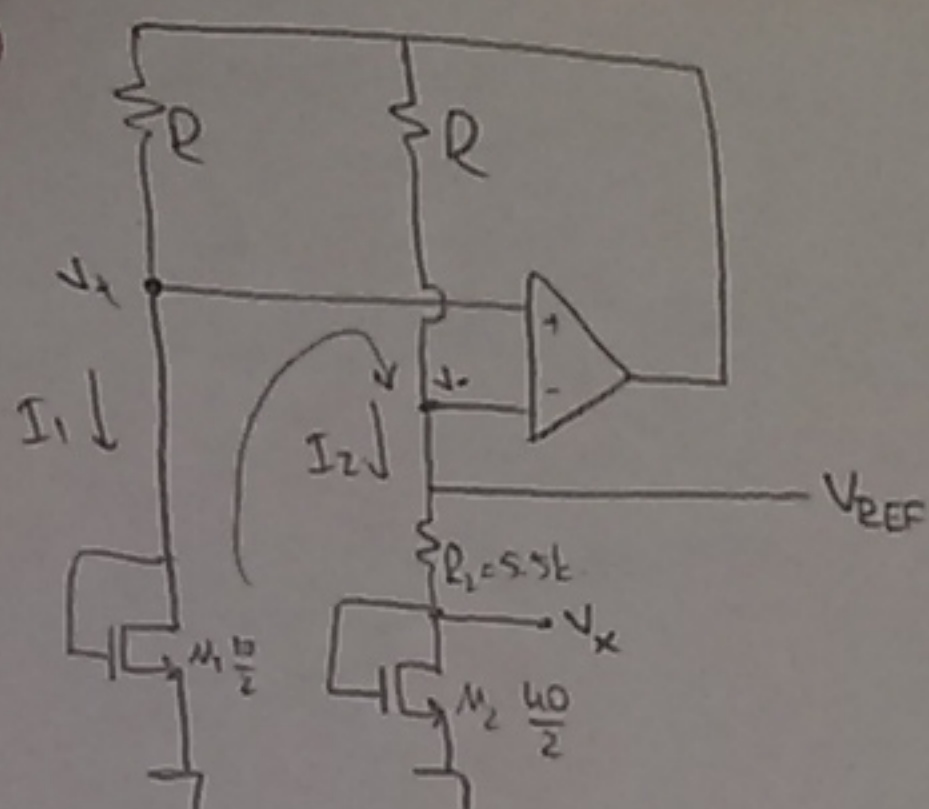

$$V_{REF} = ?$$

Assuming op-amp is ideal ; $V_+ = V_-$, $R_{in} = \infty$

$$V_{GS1} = V_{GS2} + I_2 R_2 \quad (\text{from loop eqn.})$$

$$\text{Since } V_+ = V_- \rightarrow \frac{V_{out} - V_+}{R} = \frac{V_{out} - V_-}{R} \Rightarrow I_1 = I_2$$

$$\frac{k_1}{2} \left(\frac{10}{2} \right) (V_+ - V_{T1})^2 = \frac{k_2}{2} \left(\frac{40}{2} \right) (V_x - V_{T2})^2$$

$$\text{assuming } k_1 = k_2 = k \text{ and } V_{T1} = V_{T2} = V_T$$

$$V_+ - V_T = 2(V_x - V_T) \quad (1)$$

$$V_+ - V_x = V_x - V_T \rightarrow V_- = V_+ = 2V_x - V_T$$

$$\text{also } \frac{V_+ - V_x}{R_2} = \frac{k}{2} \left(\frac{40}{2} \right) (V_x - V_T)^2$$

$$\frac{2}{k R_2 \left(\frac{W}{L} \right)_2} = V_x - V_T$$

$$V_x = \frac{2}{k R_2 \left(\frac{W}{L} \right)_2} + V_T$$

$$V_- = V_+ = 2V_x - V_T = \frac{4}{k R_2 \left(\frac{W}{L} \right)_2} + V_T = V_{REF} = \boxed{\frac{1}{27500 \text{ k}} + V_T}$$

$$R_2 = 5500 \Omega$$

$$\left(\frac{W}{L} \right)_2 = \frac{40}{2}$$

$$V_{REF} = \frac{4}{k R_2 \left(\frac{W}{L}\right)_2} + V_T$$

Here, $V_T = \frac{\sqrt{2q N_A \epsilon (2\phi_F)}}{C_{ox}} + 2\phi_F + \phi_{mb} - \frac{Q_{ss}}{C_{ox}}$

$$\phi_F = \frac{kT}{q} \ln \left[\frac{N_A \exp(E_g/2kT)}{\sqrt{N_c N_v}} \right]$$

$$\frac{dV_T}{dT} = -\frac{1}{T} \left[\frac{E_g}{2q} - \phi_F \right] \left[2 + \frac{\gamma}{\sqrt{2\phi_F}} \right] \quad \text{from Gray \& Meyer's equation 1.172}$$

Thus $\frac{dV_{REF}}{dT} = \frac{4}{k \left(\frac{W}{L}\right)_2} \frac{1}{R_2^2} \frac{dR_2}{dT} - \frac{1}{T} \left[\frac{E_g}{2q} - \phi_F \right] \left[2 + \frac{\gamma}{\sqrt{2\phi_F}} \right]$

$$\frac{dV_{REF}}{dT} = \frac{4}{k \left(\frac{W}{L}\right)_2} \frac{1}{R_2^2} \frac{dR_2}{dT} + \frac{dV_T}{dT}$$

$$TCF = \frac{1}{V_{REF}} \frac{dV_{REF}}{dT} = \frac{1}{\left[\frac{4}{k R_2 \left(\frac{W}{L}\right)_2} + V_T \right]} \left[\frac{4}{k \left(\frac{W}{L}\right)_2} \frac{1}{R_2^2} \frac{dR_2}{dT} + \frac{dV_T}{dT} \right]$$