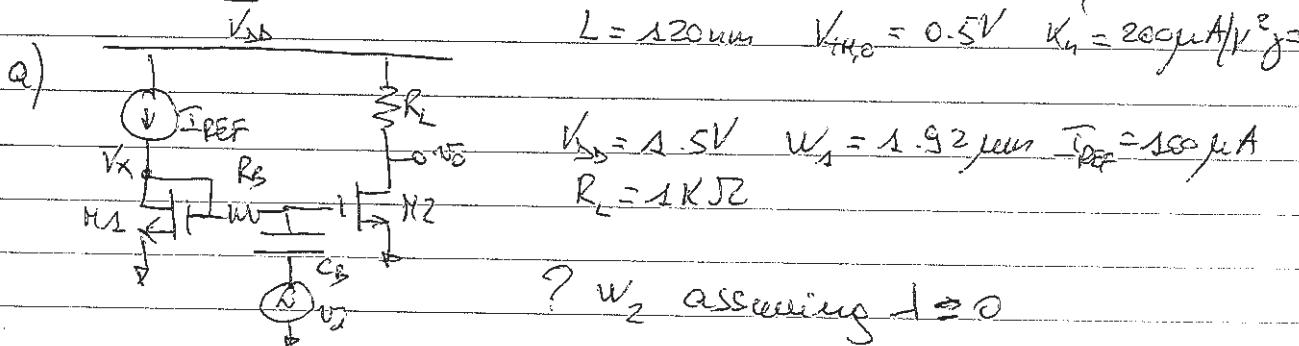


HW5 Solutions

Problem 1



$$A_{v2} = \frac{v_o}{v_i} = g_m R_L = 5 \Rightarrow g_m = 5mS = \sqrt{2K_n \left(\frac{w}{L}\right)_2 I_{D2}}$$

Call H the current mirror ratio $\left(\frac{w}{L}\right)_2 = H \left(\frac{w}{L}\right)_1 8 I_{D2} = H I_{D1}$

$$\Rightarrow g_m = \sqrt{2K_n \left(\frac{w}{L}\right)_1 I_{D1}} H^2 = \sqrt{2200\mu A/V^2 \cdot \frac{1.82\mu m}{120\text{nm}}} \cdot 100\mu A H^2$$

$$\Rightarrow H = 6.25 \quad \left(\frac{w}{L}\right)_2 = \frac{12\mu m}{120\text{nm}} \quad I_{D2} = 625\mu A$$

b) Now $\lambda = 0.4V^{-1}$? I_{D2}

$$I_{D2} = \frac{1}{2} K_n \left(\frac{w}{L}\right)_1 (V_x - V_{TH})^2 (1 + \lambda V_K) = 100\mu A$$

$$= \frac{1}{2} K_n \left(\frac{w}{L}\right)_1 [\lambda V_x^3 + V_x^2 (1 - 2\lambda V_{TH}) + V_K (\lambda V_{TH}^2 - 2V_{TH}) + V_{TH}^2] = 100\mu A$$

Can solve numerically to find $V_x = 0.72V$

$$I_{D2} = \frac{1}{2} K_n \left(\frac{w}{L}\right)_2 (V_{GS2} - V_{TH})^2 (1 + \lambda V_{SS2}) \quad V_{GS2} = V_x \quad V_{SS2} = V_0$$

$$V_0 = V_{DD} - I_{D2} R_L = V_{DD} - R_L \left[K_n \left(\frac{w}{L}\right)_2 (V_x - V_{TH})^2 (1 + \lambda V_0) \right]$$


Solving for $V_0 \rightarrow V_0 = 0.383V$

$$\Rightarrow I_{D2} = 670 \mu A$$

$$\text{Also } r_{o2} = \frac{1}{g_m2} = 3.4 K\Omega \quad g_{m2} = k_n \left(\frac{w}{L} \right)_2 (V_x - V_{th}) (1 + \beta) = 6.08 \frac{A}{V}$$

$$\Rightarrow \frac{v_o}{v_x} = g_{m2} (r_{o2} // R_L) = 4.8$$

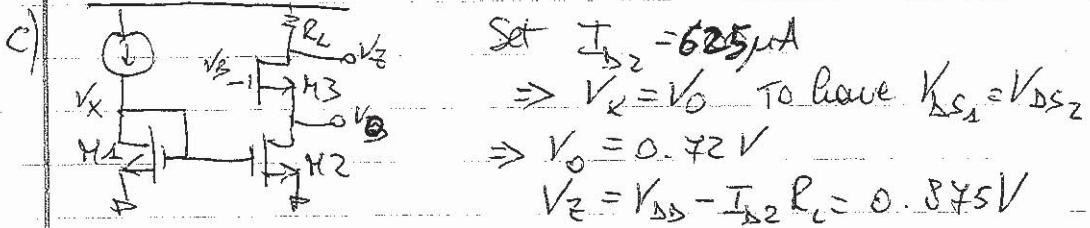I_{D2} and g_{m2} are larger than from part a) because of the channel modulation effect. On the other hand, the finite output impedance of the output transistor degrades the overall output impedance, so the gain decreases.



Now compute V_B such that M3 can drive I_{D2} ?

Assume M3 in saturation

$$I_{D3} = \frac{1}{2} k_n \left(\frac{w}{L} \right)_3 (V_{GS3} - V_{th})^2 (1 + \beta V_{DS3}) = I_{D2} = 625 \mu A$$

$$\Rightarrow V_B = \frac{1}{2} k_n \left(\frac{w}{L} \right)_3 (V_B - V_0 - V_{th})^2 (1 + \beta (V_Z - V_0)) = I_{D2}$$

$$\Rightarrow V_B = 1.44 V$$

$$\text{BUT } V_{GS_{M3}} = V_B - V_Z = 0.59 > 0.5 V > V_{th}$$

\Rightarrow Assume Triode operation


$$I_{D3} = \frac{1}{2} k_n \left(\frac{w}{L} \right)_3 [2(V_B - V_0 - V_{th})(V_Z - V_0) - (V_Z - V_0)^2] = 625 \mu A$$

$$\Rightarrow V_B = 1.465 V$$

$$V_{GS_{M3}} = V_B - V_Z = 0.615 V > V_{th} \Rightarrow \text{TRIODE!}$$

HW5 Solutions - add-on

Problem 1

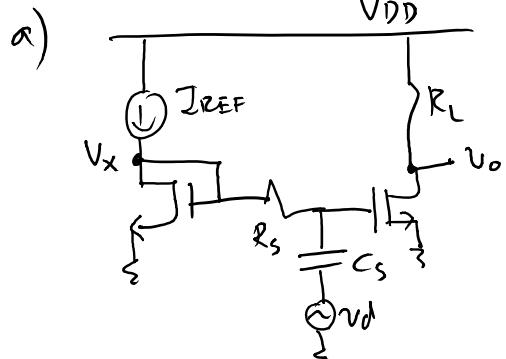

$$L = 120 \mu m, V_{th0} = 0.5 V, k_m' = 200 \frac{\mu A}{V^2}, \lambda = 0$$

$$V_{DD} = 1.5 V, W_1 = 4 \times 1.92 \mu m, I_{REF} = 100 \mu A$$

$$R_L = 1 k\Omega \quad w_2 = ? \quad \text{assuming } \lambda = 0$$

$$|A_v| = \left| \frac{V_0}{V_i} \right| = g_m R_L = 5 \Rightarrow g_m = 5 mS$$

$$g_m = \sqrt{2 k_m' \left(\frac{W}{L} \right)_2 I_{D2}}$$

$$\left(\frac{W}{L} \right)_2 = M \left(\frac{W}{L} \right)_1 \Rightarrow I_{D2} = M I_{D1}$$

$$g_m = \sqrt{2 k_m' \cdot \left(\frac{W}{L} \right)_1 \cdot I_{D1} \cdot M^2} = M \cdot \sqrt{2 k_m' \left(\frac{W}{L} \right)_1 \cdot I_{D1}}$$

$$M = \frac{g_m}{\sqrt{2 k_m' \left(\frac{W}{L} \right)_1 \cdot I_{D1}}} = 3.125$$

$$\left(\frac{W}{L} \right)_2 = \frac{24 \mu m}{120 \mu m} \Rightarrow I_{D2} = 312.5 \mu A$$

b) Now $\lambda = 0.4 V^{-1}$

$$I_{D1} = \frac{1}{2} k_m' \left(\frac{W}{L} \right)_1 (V_x - V_{th})^2 (1 + \lambda V_x) = 100 \mu A$$

Can solve numerically for V_x . $V_x = 0.612 V$

$$I_{D2} = \frac{1}{2} k_m' \left(\frac{W}{L} \right)_2 (V_x - V_{th})^2 (1 + \lambda V_o)$$

$$V_o = V_{DD} - I_{D2} R_L$$

$$V_o = \frac{V_{DD} - I_{D2, \text{SAT}} R_L}{(1 + I_{D2, \text{SAT}} \cdot R_L \cdot \lambda)} = 1.13 V$$


$$I_{D2} = 364.8 \mu A$$

HW5 Solutions - add-on

$$r_{o2} = \frac{1}{\lambda I_{D2}} = 6.8 \text{ k}\Omega \quad \left. \begin{array}{l} \\ \end{array} \right\} \Rightarrow A_V = -g_m r_{o2} R_L \| r_{o2}$$

$$g_m = k_n' \left(\frac{w}{l} \right)_2 (V_x - V_{th}) (1 + \lambda) V_0 = 6.5 \text{ mS} \\ = -5.7$$

c)

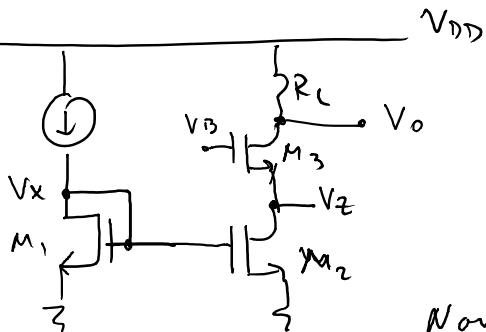

$$V_x = V_2 \quad \text{to have } V_{DS1} = V_{DS2}$$

$$V_2 = 0.612 \text{ V}$$

$$V_0 = V_{DD} - I_{D2} R_L = 1.13 \text{ V}$$


Now compute V_B such that M_3 can drive I_{D2} .

$$I_{D2} = \frac{1}{2} k_n' \left(\frac{w}{l} \right)_2 \cdot (V_B - V_2 - V_{th})^2 (1 + \lambda) \cdot (V_0 - V_2)$$

$$\Rightarrow V_B = \sqrt{\frac{2 I_{D2}}{k_n' \left(\frac{w}{l} \right)_2 \cdot (1 + \lambda) (V_0 - V_2)}} + V_{th} + V_2 = 1.235 \text{ V}$$

$$V_B - V_0 = 0.105 \text{ V} < V_{th} \Rightarrow M_3 \text{ in SAT}$$


Problem 2

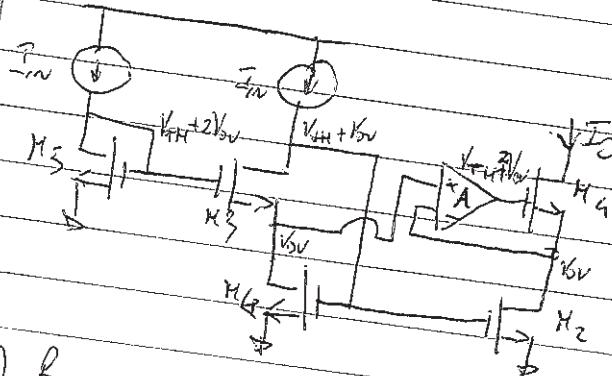

? R_{out}
? Size H_5 to minimize
the systematic gain error
at the output

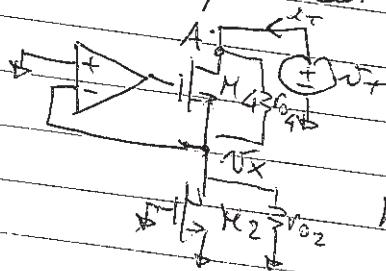a) R_{out}

To compute the output resistance, we disconnected all the input sources and apply a test source at the output. The simplified equivalent AC circuit becomes.



$$\{ v_x = i_T r_{o2} \}$$

$$KCL @ A: i_T = \frac{v_T - v_x}{r_{o4}} + g_{m4}(-Av_x - v_x)$$

$$\Rightarrow r_{o4} i_T = v_T - i_T r_{o2} - r_{o4} g_{m4} (A+s) v_x$$

$$\Rightarrow R_{out} = \frac{v_T}{i_T} = r_{o4} + r_{o2} + g_{m4} (A+s) r_{o2} r_{o4} s$$


The super-cascade configuration boosts up the output impedance by $(A+1)$ with respect to the second cascade.

b) If we size H_5 with $\left(\frac{v}{i}\right)_{H5} = \frac{1}{4} \left(\frac{v}{i}\right)_s$ we get the DC voltages reported in the figure and null systematic error $E=2$.

The OPAMP will make sure that the voltages at the drain terminals of H_4 & H_2 are the same. Note that such a choice of $\left(\frac{v}{i}\right)_{H5}$ also minimizes the required $V_{DD(CM)}$.

Problem 3

Ignore BODY EFFECT

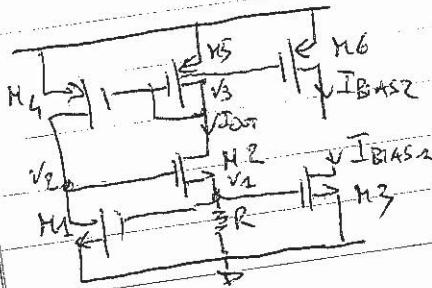

a) Compute expressions for I_{out} , I_{BIAS1} , I_{BIAS2} ($\lambda = 0$)

$$V_1 = V_{bias} = V_{ov1} + V_{TH}$$

$$V_2 = V_{GS1} + V_{AS2} = V_{ov1} + V_{ov2} + V_{TR1} + V_{TH2}$$

$$V_3 = V_{DS} - V_{ov5} - |V_{TH5}|$$

By KCL: $I_{D1} = I_{D4}$, $I_{D2} = I_{D5} = I_{out}$

By KV: $V_{ov4} = V_{ov5} = V_{ov6}$, $V_{ov1} = V_{ov3}$

let's define $K_i = \frac{1}{2} k_n (\frac{v}{l})$; $\Rightarrow I_{D1} = K_1 V_{ov1}^2$

$$\begin{aligned} &\Rightarrow I_{D1} = K_1 V_{ov1}^2 \\ &I_{D4} = K_4 V_{ov4}^2 = K_4 V_{ov5}^2 \\ &I_{D5} = I_{out} = K_5 V_{ov5}^2 \end{aligned} \quad \left. \begin{aligned} I_{D1} = I_{D4} \\ I_{D4} = \frac{K_4}{K_5} I_{out} \end{aligned} \right\} \Rightarrow \frac{K_4}{K_5} I_{out} = K_1 V_{ov1}^2$$

$$\Rightarrow V_{ov1} = \sqrt{\frac{K_4}{K_1 K_5}} I_{out}$$

$$I_{out} = \frac{V_{ov1} + V_{TH}}{R} = \frac{1}{R} \left(\sqrt{\frac{K_4}{K_1 K_5}} I_{out} + V_{TH} \right)$$

$$R I_{out} - \sqrt{\frac{K_4}{K_1 K_5}} I_{out} - V_{TH} = 0 \Rightarrow \sqrt{I_{out}} = \frac{\sqrt{\frac{K_4}{K_1 K_5}} + \sqrt{\frac{K_4}{K_1 K_5} + 4 R V_{TH}}}{2R}$$

Only the solution with the sign has physical meaning:

$$I_{OQ} = \left(\frac{\sqrt{\frac{K_4}{K_1 K_5}} + \sqrt{\frac{K_4}{K_1 K_5} + 4 R V_{TH}}}{2R} \right)^2$$

$\Rightarrow I_m$ first order, I_{OQ} doesn't depend on V_{DS} But only on circuit parameters and process values (V_{FH})

$$\begin{aligned} I_{D2} &= K_1 V_{DS2}^2 \\ I_{D3} &= K_3 V_{DS3}^2 \end{aligned} \quad \left\{ \begin{array}{l} I_{D3} = \frac{K_3}{K_5} I_{D2} = \frac{K_3}{K_1} \frac{K_4}{K_5} I_{OQ} \\ I_{BIAS1} = \frac{K_3 K_4}{K_5 K_5} \left[\frac{\sqrt{\frac{K_4}{K_1 K_5}} + \sqrt{\frac{K_4}{K_1 K_5} + 4 R V_{TH}}}{2R} \right]^2 \end{array} \right.$$

Analogously:

$$I_{BIAS2} = \frac{K_6}{K_5} \left[\frac{\sqrt{\frac{K_4}{K_2 K_5}} + \sqrt{\frac{K_4}{K_2 K_5} + 4 R V_{TH}}}{2R} \right]^2$$

Now, plugging in numbers

$$K_1 = \frac{1}{2} \cdot 200 \frac{\mu A}{V^2} \cdot 50 = 5 \frac{\mu A}{V^2} \quad K_2 = \frac{1}{2} \cdot 200 \frac{\mu A}{V^2} \cdot 25 = 25 \frac{\mu A}{V^2}$$

$$K_3 = \frac{1}{2} \cdot 200 \frac{\mu A}{V^2} \cdot 125 = 12.5 \frac{\mu A}{V^2} \quad K_4 = \frac{1}{2} \cdot 100 \frac{\mu A}{V^2} \cdot 25 = 1.25 \frac{\mu A}{V^2}$$

$$K_5 = \frac{1}{2} \cdot 100 \frac{\mu A}{V^2} \cdot 50 = 2.5 \frac{\mu A}{V^2} \quad K_6 = \frac{1}{2} \cdot 100 \frac{\mu A}{V^2} \cdot 62 = 3.1 \frac{\mu A}{V^2}$$

$$I_{OQ} = \frac{\sqrt{\frac{1.25}{5 \cdot 2.5 \cdot 0.5} + \sqrt{\frac{1.25}{5 \cdot 2.5 \cdot 0.5} + 4 \cdot 1.75 \cdot 0.5 V}}}{2 \cdot 1.75 K_2} = 0.4 \mu A$$

$$I_{D2} = I_{D5} = I_{OQ} = 0.4 \mu A \Rightarrow V_{DS2} = 0.4 V \quad V_{DS5} = 0.4 V$$

$$I_{D3} = I_{D4} = \frac{K_4}{K_5} I_{OQ} = 0.2 \mu A \rightarrow V_{DS3} = 0.2 V \quad V_{DS4} = 0.4 V$$

$$I_{BIAS1} = \frac{K_3}{K_2} \frac{K_4}{K_5} I_{OQ} = \frac{12.5}{5} \frac{1.25}{2.5} \cdot 0.4 \mu A = 0.5 \mu A$$

$$I_{BIAS2} = \frac{K_6}{K_5} I_{OQ} = 0.496 \mu A$$

$$V_1 = V_{DS1} + V_T = 0.7V \quad V_2 = V_{DS2} + V_{DS3} + 2V_T = 1.6V$$

$$V_3 = V_{DD} - V_{DS5} - V_T = 2.1V$$

\Rightarrow all Transistors are ~~are~~ in saturation

$$g_m = 2KbV$$

$$\Rightarrow g_{m1} = 2mS \quad g_{m2} = mS \quad g_{m3} = 5mS \quad g_{m4} = 1mS$$

$$g_{m5} = 2mS \quad g_{m6} = 2.48mS$$


- b) We assume the DC values don't change \Rightarrow when we set $A = 0.05V^{-1}$, but even Transistors have a small signal output impedance.

$$r_{o1} = \frac{1}{AIB_1}$$

$$r_{o1} = 100K\Omega \quad r_{o2} = 50K\Omega \quad r_{o3} = 40K\Omega \quad r_{o4} = 100K\Omega$$

$$r_{o5} = 50K\Omega \quad r_{o6} = 40.3K\Omega$$

We use the following small signal model:

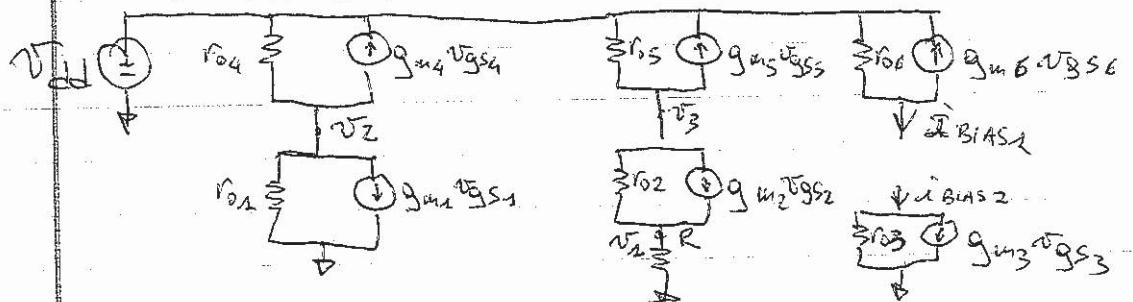

$$V_{GS1} = V_{GS3} = V_1$$

$$V_{GS2} = V_2 - V_1$$

$$V_{GS4} = V_{GS5} = V_{DS6} = V_3 - V_{DD}$$

$$\begin{aligned} \text{KCL @ 2: } & \frac{v_2}{r_{01}} + g_{m1} v_{GS1} + \frac{v_2 - v_{dd}}{r_{04}} + g_{m4} v_{GS4} = 0 \\ \text{KCL @ 3: } & \frac{v_3 - v_2}{r_{02}} + g_{m2} v_{GS2} + \frac{v_3 - v_{dd}}{r_{05}} + g_{m5} v_{GS5} = 0 \\ \text{KCL @ 1: } & \frac{v_1}{R} + \frac{v_1 - v_3}{r_{02}} - g_{m2} v_{GS2} = 0 \end{aligned}$$

$$\left(\begin{array}{ccc} g_{m1} & \frac{1}{r_{01}} + \frac{1}{r_{04}} & g_{m4} \\ -g_{m2} - \frac{1}{r_{02}} & g_{m2} & g_{m5} + \frac{1}{r_{02}} + \frac{1}{r_{05}} \\ \frac{1}{R} + \frac{1}{r_{02}} + g_{m2} & -g_{m2} & \frac{1}{r_{02}} \end{array} \right) \left(\begin{array}{c} v_2 \\ v_3 \\ v_1 \end{array} \right) = \left(\begin{array}{c} g_{m4} + \frac{1}{r_{04}} \\ g_{m5} + \frac{1}{r_{05}} \\ 0 \end{array} \right) v_{dd}$$

$$\left(\begin{array}{ccc} 2 & 0.02 & 1 \\ -2.02 & 2 & 2.04 \\ 2.593 & -2 & -0.02 \end{array} \right) \left(\begin{array}{c} v_2 \\ v_3 \\ v_1 \end{array} \right) = \left(\begin{array}{c} 1.03 \\ 2.02 \\ 0 \end{array} \right) v_{dd}$$

$$\Rightarrow \left(\begin{array}{c} v_1 \\ v_2 \\ v_3 \end{array} \right) = \left(\begin{array}{c} 5.851 \\ -2.4 \\ 998.3 \end{array} \right) \cdot 10^{-3} v_{dd}$$

$$\Rightarrow i_{out} = \frac{v_1}{R} = \frac{5.851 \cdot 10^{-3}}{1.75 k\Omega} v_{dd} \Rightarrow \frac{1}{v_{dd}} = 3.343 \cdot 10^{-3} \mu S$$

\Rightarrow You see that for even 100 mV change in V_{ds} , I_{out} just changes for $\Delta i_{out} = 0.3 \mu A$


$$i_{BIAS1} = g_{m3} v_3 \Rightarrow \frac{i_{BIAS1}}{v_{dd}} = 5 mS + 5.851 \cdot 10^{-3} = 29.255 \cdot 10^{-3} \mu S$$

$$i_{BIAS2} = g_{m6} (v_3 - v_{dd}) = 2.48 mS + 1.656 \cdot 10^{-3} v_{dd}$$


$$\Rightarrow \frac{i_{BIAS2}}{v_{dd}} = 4.1 \cdot 10^{-3} \mu S$$

HW5 Solutions - add-on

Problem 3 - simplification for (3b)

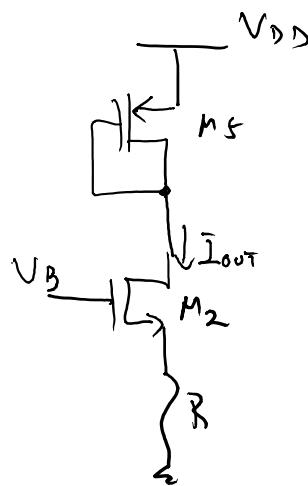

small-signal
⇒

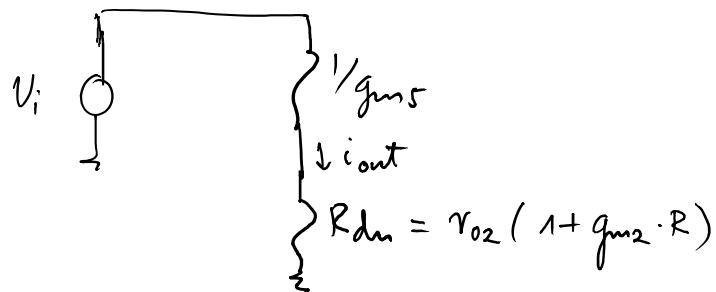

$$\frac{i_{out}}{V_i} = \frac{1}{\frac{1}{g_{m5}} + r_o2 / (1 + g_{m2}R)}$$

$$= 4.4 \mu S$$

$$g_{m5} = 2 \mu S$$

$$r_o2 = 50 k\Omega$$


$$R = 1.75 k\Omega$$

$$g_{m3} = 5 \mu S$$

$$\frac{i_{bias2}}{v_i} = \frac{\left(\frac{w}{l}\right)_c}{\left(\frac{w}{l}\right)_s} \cdot \frac{i_{out}}{V_i} = 5.45 \mu S$$

$$\frac{i_{bias1}}{v_i} = \frac{R}{\frac{1}{g_{m5}} + R_{dm}} \cdot g_{m3} = 31.8 \mu S$$

Problem 4

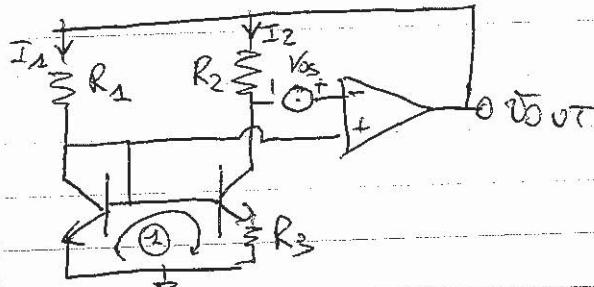

$$R_1 = R_3 = 1 \text{ k}\Omega$$

$$I_{S1} = 10^{-15} \text{ A}, I_{S2} = 10^{-15} \cdot 8 \text{ A}$$

$$B_F \rightarrow \infty, V_A \rightarrow \infty$$

a) First, we complete the expression for V_{out}

$$\text{KVL @ ①: } V_{BE1} = V_{BE2} + I_2 R_3 \quad (\dagger)$$

$$I_1 = \frac{V_{out} - V_{BE1}}{R_1} \quad I_2 = \frac{V_{out} - V_{BE1} + V_{OS}}{R_2}$$

$\Rightarrow (*)$ becomes:

$$V_T \ln\left(\frac{I_1}{I_2} \cdot \frac{I_{S2}}{I_{S1}}\right) = \frac{R_3}{R_2} (V_{out} - V_{BE1} + V_{OS})$$

$$V_T \ln\left[8 \frac{R_2}{R_1} \cdot \frac{V_0 - V_{BE1}}{V_0 - V_{BE1} + V_{OS}} \right] = \left(\frac{R_3}{R_2} \right) (V_{out} - V_{BE1} + V_{OS})$$

$$\Rightarrow V_0 = V_{BE1} + \frac{R_2}{R_3} V_T \ln\left[8 \frac{R_2}{R_1} \right] - V_{OS} + \frac{R_2}{R_3} V_T \ln\left[\frac{V_0 - V_{BE1}}{V_0 - V_{BE1} + V_{OS}} \right]$$

Now we use the approximation $\ln(1+x) \approx x \quad x \approx 0$

$$-\frac{R_2}{R_3} V_T \ln\left[\frac{V_0 - V_{BE1} + V_{OS}}{V_0 - V_{BE1}} \right] \approx -\frac{R_2}{R_3} V_T \frac{V_{OS}}{V_0 - V_{BE1}}$$

$$(*) \Rightarrow V_0 = V_{BE1} + \frac{R_2}{R_3} V_T \ln\left[8 \frac{R_2}{R_1} \right] - \underbrace{\left(V_{OS} + \frac{R_2}{R_3} V_T \frac{V_{OS}}{V_0 - V_{BE1}} \right)}_{\epsilon = \text{ERROR TERM}}$$

For $V_{OS} = 0$, we set $\frac{\partial V_{out}}{\partial T} = 0$

$$\frac{\partial V_{out}}{\partial T} = \underbrace{\frac{\partial V_{BE}}{\partial T} + \frac{R_2}{R_3} \ln\left(\beta \frac{R_2}{R_1}\right)}_{-2 \frac{mV}{K} \text{ H.GAIN} = 23} \frac{\partial V_T}{\partial T} + 0.086 \frac{mV}{K} \quad (\star \star)$$

Plugging in the numerical values, we get:

$$R_2 \ln\left(\beta \frac{R_2}{R_1}\right) = 23$$

$$\Rightarrow R_2 \approx 6 \text{ k}\Omega \quad (\text{solving numerically})$$

We can now compute the target voltage:

$$V_{out}^{\text{TARGET}} = V_{BE1} + \frac{R_2}{R_3} V_T \ln\left[\beta \frac{R_2}{R_1}\right] = 0.7V + 23 \cdot 26 \mu V - 1.293V$$

Unfortunately at this time the offset will create an error in the calibration of R_2 .

We make the following approximation to simplify the expression for

$$E = V_{OS} \left(1 + \frac{R_2}{R_3} \frac{V_T}{V_0 - V_{BE1}} \right) \approx V_{OS} \left(1 + \frac{R_2}{R_3} \frac{V_T}{\frac{R_2}{R_3} V_T \ln\left(\beta \frac{R_2}{R_1}\right)} \right)$$

where we used $V_0 - V_{BE1} \approx \frac{R_2}{R_3} V_T \ln\left(\beta \frac{R_2}{R_1}\right)$ from $(\star \star)$

$$\Rightarrow E = V_{OS} \left(1 + \frac{1}{\ln(48)} \right)$$

At biasing time, the gain H (***) will be

Set by:

$$V_{out} = V_{BE1} + H V_{target} - \epsilon = V_{out}^{target}$$

$$0.7V - \epsilon + H \cdot 26mV = 1.298$$

$$\Rightarrow H = \frac{V_{out}^{target} - V_{BE1} + \epsilon}{V_T} \quad (\text{***})$$

$\cancel{V_T} \rightarrow \text{error term}$


The gain error will translate in a residual Temperature coefficient

$$\frac{\partial H_{\text{err}}}{\partial T} = \frac{\epsilon}{V_T} \cdot \frac{\partial V_T}{\partial T} = \frac{\epsilon}{V_T} \cdot \frac{K}{9} \cdot \frac{1}{T} = \frac{\epsilon}{T}$$
$$= \frac{300mV(1 + \alpha(48))}{300K} = 125 \frac{\mu V}{K}$$

$$TC_F = \frac{1}{V_{out}} \cdot \frac{\partial V_{out}}{\partial T} = 96 \frac{\text{ppm}}{K}$$

- b) If $\epsilon > 0$ (****) shows that the trimming will overcompensate the gain H . Since this gain is applied to the term in (****) with positive temperature coefficient ΔV_{BE1} , the TC_F will be positive.
On the other hand, if $\epsilon < 0$ the trimming will under compensate H and TC_F will be negative.

Problem 5

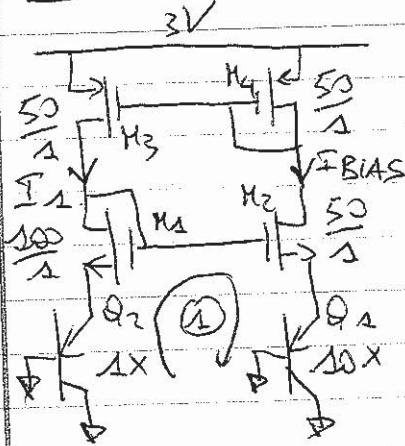

$$|V_{TH}| = 0.5V$$

$$K_n' = 200 \mu A/V^2$$

$$K_p' = 200 \mu A/V^2$$

a) ? I_{BIAS}

$$KVL @ ①: V_{EB2} + V_{GS1} - V_{GS2} - V_{EB1} = 0$$

$$\Rightarrow V_{GS1} - V_{GS2} = V_T \ln\left(\frac{I_{BAS}}{10 I_{S2}} \cdot \frac{I_{S2}}{I_{BAS}}\right) = -V_T \ln(10) - (*)$$

where we assumed $I_{BIAS} = I_S$ (enforced by current mirror)

$$I_{BIAS} = I_S$$

$$\Rightarrow \frac{1}{2} K_n \left(\frac{w}{L}\right)_1 (V_{GS1} - V_{TH})^2 = \frac{1}{2} K_n \left(\frac{w}{L}\right)_2 (V_{GS2} - V_{TH})^2$$

$$\sqrt{2} (V_{GS1} - V_{TH}) = V_{GS2} - V_{TH}$$

Combining with (*)


$$V_{GS1} = \frac{V_T \ln(10)}{\sqrt{2-1}} + V_{TH}$$

$$\Rightarrow I_{BIAS} = \frac{1}{2} K_n \left(\frac{w}{L}\right)_2 \left[\frac{\sqrt{2} V_T \ln(10)}{\sqrt{2-1}} + V_{TH} - V_{TH} \right]^2 = 209 \mu A$$

$$I_{BIAS} = \frac{1}{2} K_n \left(\frac{w}{L}\right)_2 \sqrt{V_T^2 \frac{\ln^2(10)}{(\sqrt{2}-1)^2}}$$

$$b) \frac{\partial I_{BIAS}}{\partial T} = 2 k_n \left(\frac{u}{L} \right)_2 \frac{k^2}{q^2} \frac{e^2 (10)}{(12-1)^2} \cdot T$$

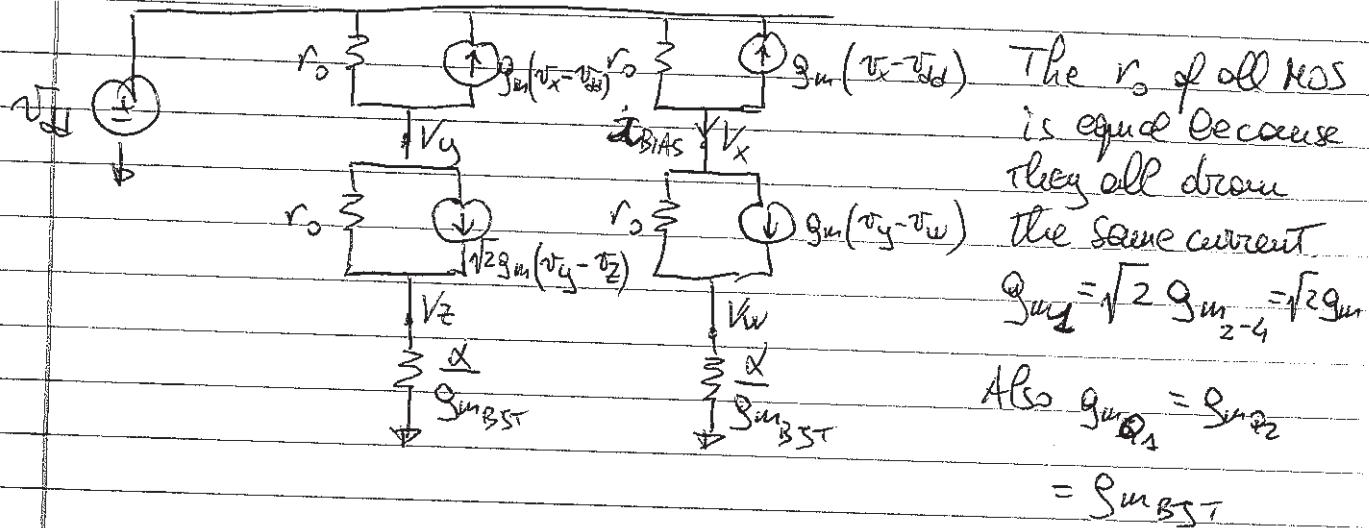c) We consider the following second signal circuit:



We write KCL at the four nodes marked in the ~~circuit~~ circuit. Our goal is to compute $i_{BIAS} = f(v_{dd})$

$$\text{KCL @ Y: } \frac{v_{dd} - v_y}{r_o} - g_m(v_x - v_{dd}) - \frac{v_y - v_z}{r_o} - g_m(v_y - v_z) = 0$$

$$\text{KCL @ Z: } \frac{v_y - v_z}{r_o} + \sqrt{2} g_m(v_y - v_z) - \frac{g_{m_{BSI}}}{\alpha} v_z = 0$$

$$\text{KCL @ X: } \frac{v_{dd} - v_x}{r_o} - g_m(v_x - v_{dd}) - \frac{v_x - v_w}{r_o} - g_m(v_y - v_w) = 0$$

$$\text{KCL @ W: } \frac{v_x - v_w}{r_o} + g_m(v_y - v_w) - \frac{g_{m_{BSI}}}{\alpha} v_w = 0$$

Now put in matrix format:

$$\begin{pmatrix}
 q_m & \frac{2}{r_0} + g_m & -\frac{1}{r_0} g_m & 0 \\
 0 & -\frac{1}{r_0} = \sqrt{2} g_m & \sqrt{2} g_m + \frac{1}{r_0} + \frac{g_{BAS}}{2} & 0 \\
 \frac{2}{r_0} + g_m & g_m & 0 & -\frac{1}{r_0} g_m \\
 -\frac{1}{r_0} & -g_m & 0 & \frac{1}{r_0} + \frac{g_{BAS}}{2} + g_m
 \end{pmatrix} \begin{pmatrix} v_x \\ v_y \\ v_z \\ v_w \end{pmatrix}$$

$$= \begin{pmatrix} \frac{1}{r_0} + g_m \\ 0 \\ \frac{1}{r_0} + g_m \\ 0 \end{pmatrix} v_{dd}$$

$$r_0 = \frac{1}{2I_D} = 95 \text{ kJ} \quad g_m = \sqrt{2K_n \frac{W}{L} I_D} = 2 \mu S$$

$$g_{BAS} = \frac{I_D}{V_t} = 8 \mu S$$

$$\begin{pmatrix}
 2m & 2.83m & -2.83m & 0 \\
 0 & -2.83m & 10.83m & 0 \\
 2.02m & 2m & 0 & -2.02m \\
 0.02m & -2m & 0 & 10.02m
 \end{pmatrix} \begin{pmatrix} v_x \\ v_y \\ v_z \\ v_w \end{pmatrix} = \begin{pmatrix} 2.02m \\ 0 \\ 2.02m \\ 0 \end{pmatrix}$$


$$\begin{pmatrix} v_x \\ v_y \\ v_z \\ v_w \end{pmatrix} = \begin{pmatrix} 0.96 \\ 0.062 \\ 0.01 \\ 0.0074 \end{pmatrix} v_{dd}$$

$$i_{BAS} = \frac{g_{m_{BAS}} v_u}{2} = 59.2 \cdot 10^{-6} v_{dd} \quad \frac{d_{BAS}}{v_{dd}} = 59.2 \cdot 10^6 S$$


As expected the ~~sigma~~ sensitivity is POSITIVE.

HW5 Solutions - add-on

Problem 5 - simplification for (5c)

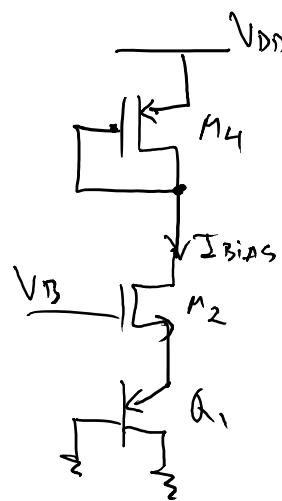

=>

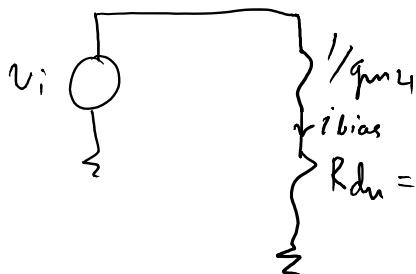

$$\frac{i_{bias}}{v_i} = \frac{1}{\frac{1}{gm_M4} + R_{din}} = 6.4 \mu S$$

$$r_{02} = 95 \text{ m}\Omega$$

$$gm_2 = 2 \text{ mS}$$

$$gm_{BJT} = 8 \text{ mS}$$

$$R_{din} = r_{02} \left(1 + gm_2 \cdot \frac{\alpha_f}{gm_{BJT}} \right)$$