



Common Mode Feedback

Q1. Fig. 1 shows common mode feedback network.

- Obtain common mode output expression in terms of  $I_D$ ,  $V_{b4}$  and transistor parameters.
- Define possible handicaps of these type of CMFB networks


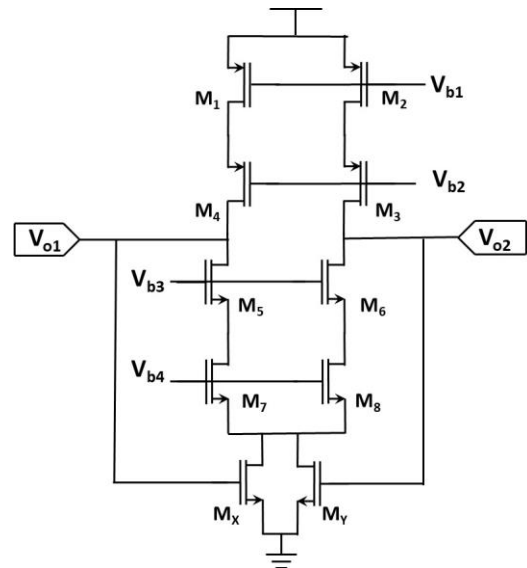
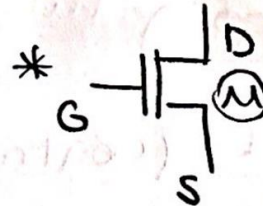


Fig 1. CMFB network

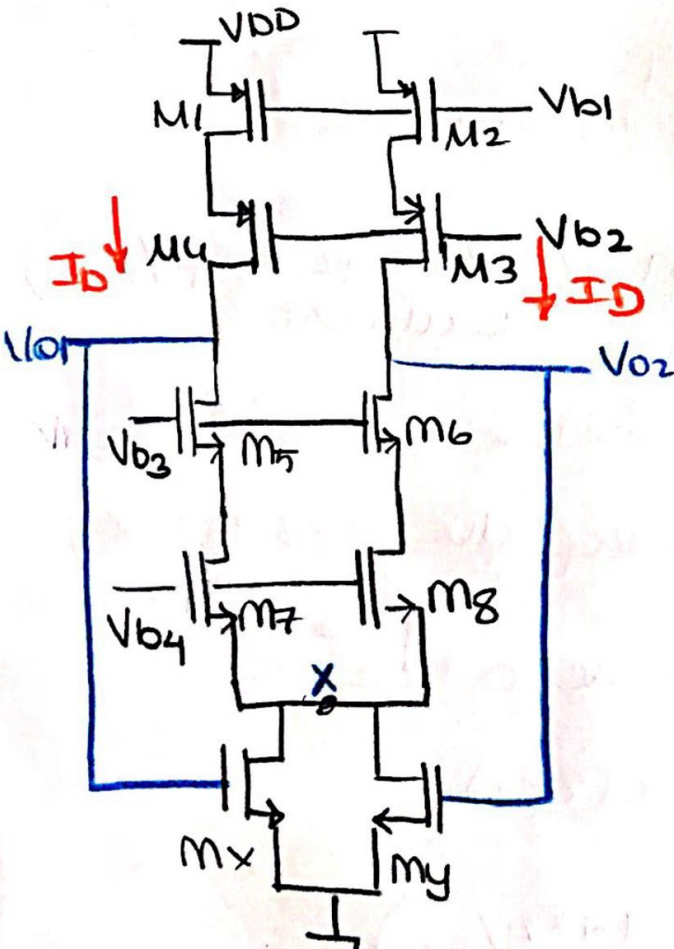

If  $\mu$  operates in linear region, it can be assumed as a resistor

$$I_D = K_N [(V_{GS} - V_{TN}) V_{DS} - \frac{V_{DS}^2}{2}]$$

If  $V_{DS}$  is small.

$$I_D = K_N [(V_{GS} - V_{TN}) V_{DS}]$$

$$\rightarrow R_{ON} = \frac{V_{DS}}{I_D} = \frac{1}{K_N (V_{GS} - V_{TN})}$$

In our circuit,  $M_X$  &  $M_Y$  can be used as resistors.

$$I_D = K_N \left[ (V_{GSX} - V_{TN}) V_{DSX} - \frac{V_{DSX}^2}{2} \right]$$

$$\Rightarrow R_{ONX} = \frac{1}{\underset{\substack{\uparrow \\ \mu n C_{OX} (W/L)_{X,Y}}}{K_N (V_{GSX} - V_{TN})} \overset{\substack{\uparrow \\ V_{O1}}}{V_{DSX}}}$$

$$R_{ONX} = \frac{1}{\mu n C_{OX} (W/L)_X (V_{O1} - V_{TN})}$$

$$R_{ONY} = \frac{1}{\mu n C_{OX} (W/L)_Y (V_{O2} - V_{TN})}$$

At node X:  $R_{ONX} \parallel R_{ONY}$

$$(W/L)_X = (W/L)_Y$$

$$R_{ONX} \parallel R_{ONY} = \frac{1}{\frac{1}{\mu n C_{OX} (W/L)_X (V_{O1} - V_{TN})} + \frac{1}{\mu n C_{OX} (W/L)_X (V_{O2} - V_{TN})}}$$

$$R_{ONX} \parallel R_{ONY} = \frac{1}{\mu n C_{OX} (W/L)_{X,Y} (V_{O1} + V_{O2} - 2V_{TN})} = \frac{V_{DD} - V_{GS7}}{2I_D}$$

(Due to  $M_7$ )

$$\rightarrow V_{O1} + V_{O2} = \frac{2I_D}{\mu n C_{OX} (W/L)_{X,Y} (V_{DD} - V_{GS7})} + 2V_{TN} \quad (I)$$

$I_D$  flows through  $M_7$

$$I_D = \frac{K_{N7}}{2} (V_{GS7} - V_{TN})^2 \rightarrow V_{GS7} = \sqrt{\frac{2I_D}{\mu n C_{OX} (W/L)_7}} + V_{TN} \quad (II)$$

Using (I) and (II)

Since circuit is symmetric  $V_{O1} = V_{O2}$

$$V_{O1} = V_{O2} = \frac{I_D}{\mu_n C_{ox} \left( \frac{W}{L} \right)_{X,Y} \left( V_{b4} - \sqrt{\frac{2I_D}{\mu_n C_{ox} \left( \frac{W}{L} \right)_Z}} - V_{TN} \right)} + V_{TN}$$

b) There are some drawbacks of CMFB.

I.) Output voltage is a function of device parameters.

There might be differences between the components during manufacturing.

II.) Voltage drop on  $M_X$  and  $M_Y \rightarrow R_{OX} \parallel R_{OY}$  limits the output voltage swing.

III.) In order to improve the voltage drop on  $X$  &  $Y$ , their size can be increased. However, in that case capacitance appears at the output.