





**ELECTRICAL AND ELECTRONICS
ENGINEERING
DEPARTMENT**

**4x4 Keypad Module
with
8 LEDs and 4 Switches**



Banggood.com

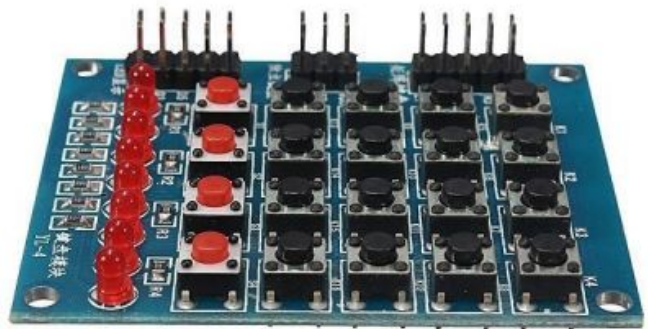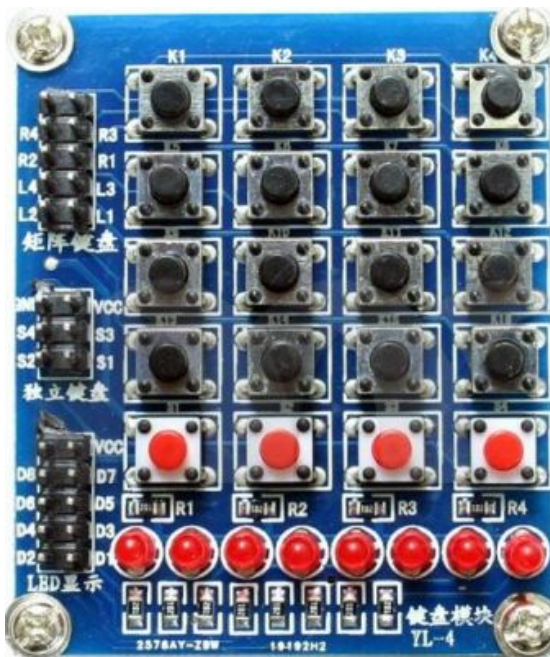Datasheet - 4x4 Keypad Module with 8 LEDs and 4 Switches



Banggood.com

Figure 1: Keypad module to be used in the experiment

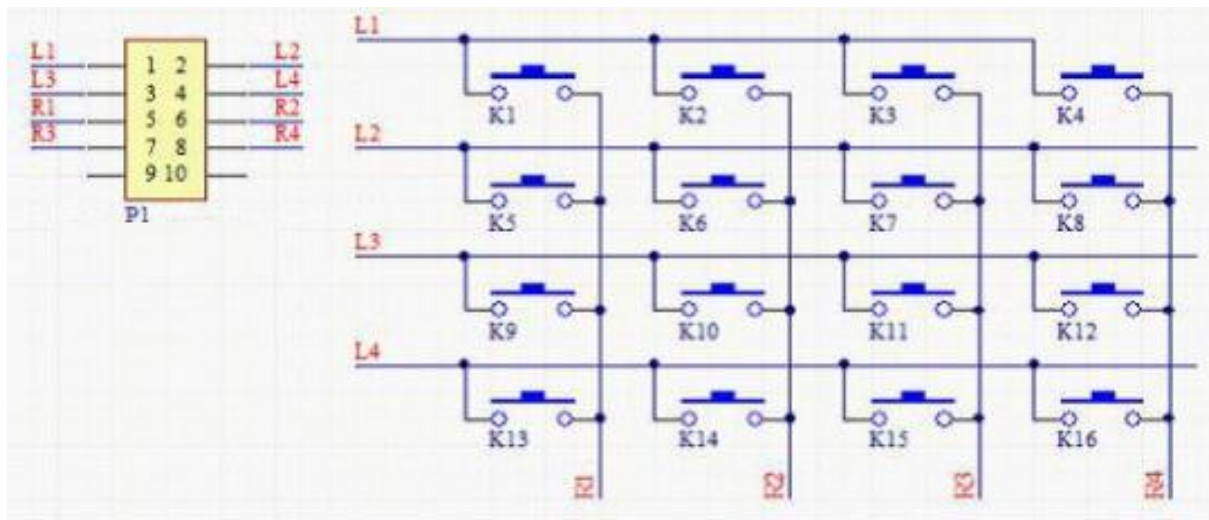


Figure 2: Circuit diagram of 4x4 Keypad

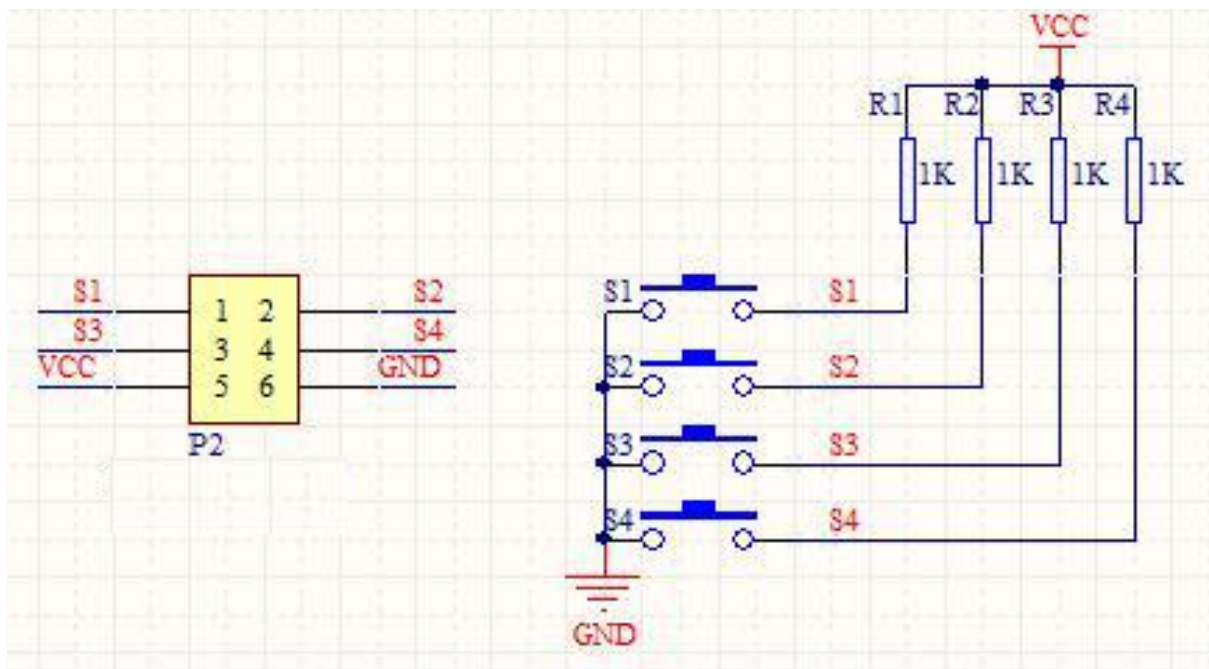


Figure 3: Circuit diagram of 4 Push Buttons

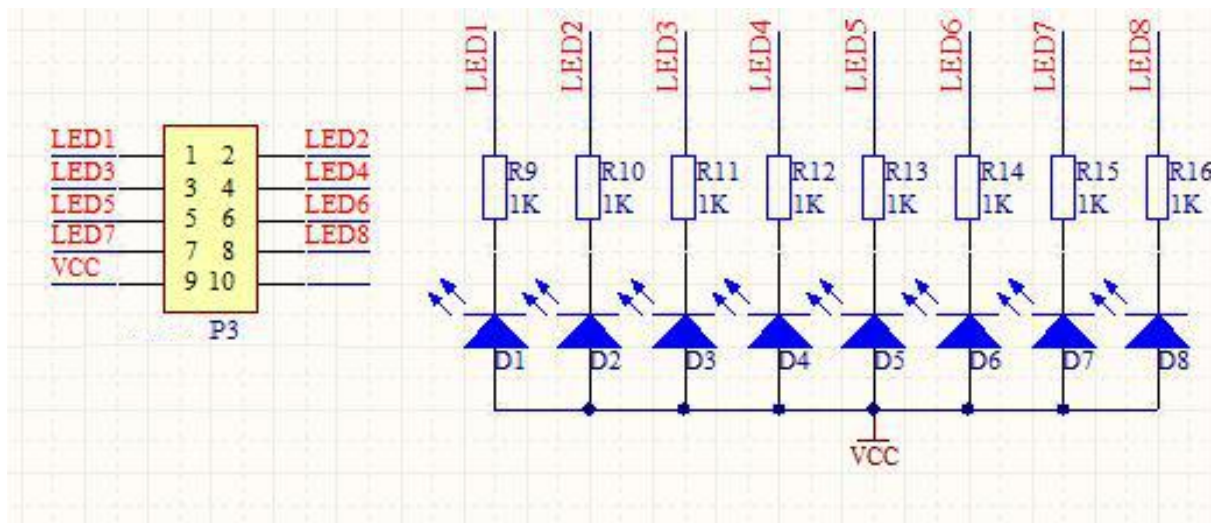


Figure 4: Circuit diagram of 8 LEDs