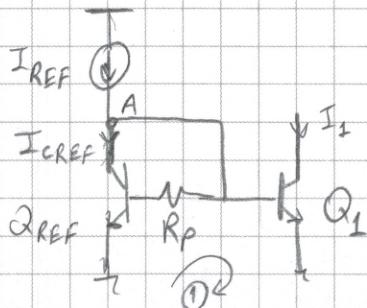


EE414 - Introduction to Analog Integrated Circuits
Take Home Exam - 2

Problem 1



$$I_1 = 1.1 I_{1,NOM}$$

First compute $I_{1,NOM}$, i.e. I_1 with $R_p=0$

$$I_{1,NOM} = I_{REF} \frac{\beta}{\beta+2} \Rightarrow I_1 = 1.1 I_{REF} \frac{\beta}{\beta+2}$$

Now Let's consider R_p :

$$\text{KVL @ Loop ①: } V_{BE} + \frac{I_{CREF}}{\beta} R_p = V_{BE1}$$

$$V_T \ln \left(\frac{I_1}{I_S} \right) - V_T \ln \left(\frac{I_{CREF}}{I_S} \right) = \frac{I_{CREF}}{\beta} R_p$$

$$R_p = \frac{\beta}{I_{CREF}} V_T \ln \left(\frac{1.1 I_{REF} \frac{\beta}{\beta+2}}{I_{CREF}} \right) \quad \dots \quad (1)$$

$$\text{KCL @ A: } I_{REF} = I_{CREF} + \frac{I_{CREF}}{\beta} + \frac{I_1}{\beta}$$


$$I_{CREF} = I_{REF} \frac{\left(1 - \frac{1.1}{\beta(\frac{\beta+2}{\beta})} \right)}{1 + \frac{1}{\beta}} = \frac{\beta(\beta+0.9)}{(\beta+1)(\beta+2)} I_{REF}$$

Now substitute back in (1)

$$R_p = \frac{(\beta+1)(\beta+2)}{\beta+0.9} \frac{V_T}{I_{REF}} \ln \left[\frac{1.1 \beta(\beta+1)(\beta+2)}{\beta(\beta+2)(\beta+0.9)} \right]$$

$$\Rightarrow R_p = \boxed{\frac{(\beta+1)(\beta+2)}{\beta+0.9} \frac{V_T}{I_{REF}} \ln \left[\frac{1.1 (\beta+1)}{\beta+0.9} \right]}$$

Problem 2:

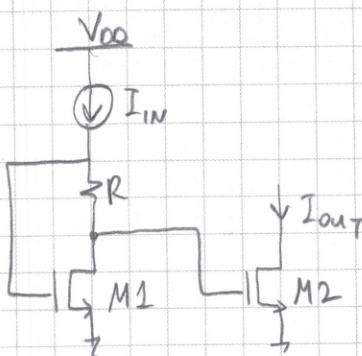

$$I_{out} = 0.1 \text{ mA} \quad \left(\frac{w}{l}\right)_1 = \left(\frac{w}{l}\right)_2$$

a) $I_{in} = 1 \text{ mA}$

We need to determine the values range of $\left(\frac{w}{l}\right)_1$ and for each value of $\left(\frac{w}{l}\right)_1$ compute the corresponding value of R that guarantees an output current of $I_{out} = 0.1 \text{ mA}$

From Gray & Meyer :

$$I_{out} = \frac{k'}{2} \left(\frac{w}{l}\right)_1 \left(\sqrt{\frac{2I_{in}}{k'(\frac{w}{l})}} - RI_{in} \right)^2 \quad \dots \quad (1)$$

Solving for R;

$$R = \frac{\frac{2I_{in}}{k'(\frac{w}{l})} - \sqrt{\frac{2I_{out}}{k'(\frac{w}{l})}}}{I_{in}} \quad \dots \quad (2)$$

To operate in saturation: $V_{GD_1} = R I_{IN} \leq V_{TH} = 0.5V$... ③

$$R \leq \frac{V_{TH}}{I_{IN}}$$

$$\frac{\sqrt{\frac{2I_{IN}}{K'(w/L)}} - \sqrt{\frac{2I_{out}}{K'(w/L)}}}{I_{IN}} \leq \frac{V_{TH}}{I_{IN}} \Rightarrow \left(\frac{w}{L}\right) \leq 1.663$$

\Rightarrow From Gray & Meyer; To operate in strong inversion;

$$V_{out} = \sqrt{\frac{2I_{IN}}{K'(w/L)}} \geq 3V_T = 78mV \Rightarrow \left(\frac{w}{L}\right) \geq 0.018$$

\Rightarrow Now we can compute corresponding R range by using eqn. ②.

$$0.018 \leq \left(\frac{w}{L}\right) \leq 1.663$$

$$53k\Omega \leq R \leq 496k\Omega$$

b) Now size $R=10k\Omega$ and compute the range of $\frac{w}{L}$ and I_{IN} to maintain $\frac{w}{L}$ in strong inversion and saturation.

We use the same constraints as before,

From ③ $I_{IN} \leq 50mA$

When we put upper condition to the eqn ②;

$$\left(\frac{w}{L}\right) \leq 1.825$$

\Rightarrow To operate in strong inversion

$$\sqrt{\frac{2I_{IN}}{K'(w/L)}} > 78mV \Rightarrow I_{IN} > 78 \times 10^3 \sqrt{\frac{w}{L}}$$


\Rightarrow when we put it into eqn ②

$$\frac{w}{L} \geq 0.34, I_{IN} \geq 0.2mA$$


$$0.34 \leq \frac{w}{L} \leq 1.825$$

$$0.2mA \leq I_{IN} \leq 50mA$$

Problem 3:

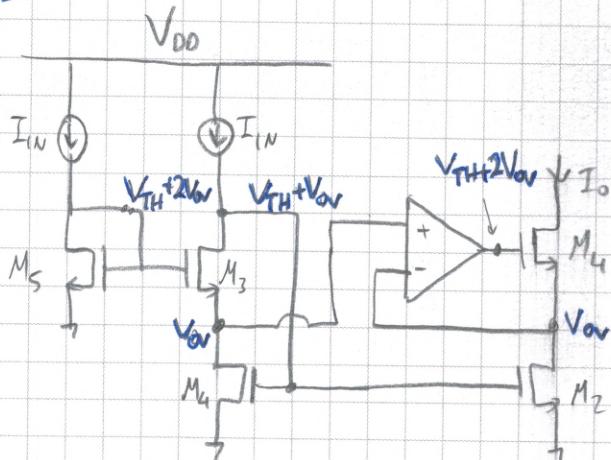

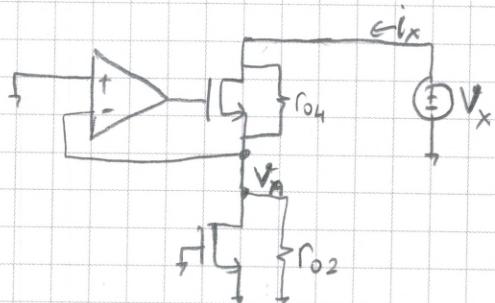a) To compute the output resistance, we disconnected all the input sources and apply a test source at the output. The simplified equivalent circuit becomes.



$$V_A = i_A R_{02} \quad \dots \dots \dots \quad (1)$$

$$i_x = \frac{V_x - V_A}{R_{02}} + g_m u (-AV_A - V_A) \quad \dots \dots \dots \quad (2)$$

Combine (1) & (2)

$$R_{04} i_x = V_x - i_A R_{02} = g_m R_{04} (A+1) R_{02} i_x$$


$$R_{out} = \frac{V_x}{i_x} = R_{02} + R_{04} + g_m R_{04} R_{02} (A+1) \approx g_m R_{04} R_{02} (A+1)$$

\Rightarrow The super-cascode configuration boostes-up the output impedance by $(A+1)$ with respect to the regular cascode.

b) If we size M_5 with $(\frac{w}{l})_5 = \frac{1}{4}(\frac{w}{l})$ we get the DC voltages reported in the figure and systematic error $E=0$.

The OPAMP will make sure that the voltages at the drain terminals of M_4 & M_2 are the same. Note that such a choice of $(\frac{w}{l})_5$ also minimizes the required $V_{out,MIN}$.

Problem 4:

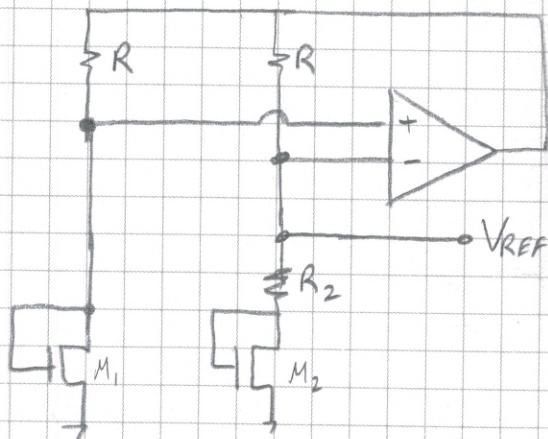

$$R_2 = 5.5 K\Omega$$

$$W_1 = W$$

$$W_2 = K \cdot W_1 \Rightarrow K = 4$$

You can see from the left side of the circuit that V_{REF} is equal to the gate-to-source voltage of M_1 . This results because the amplifier feedback holds its inputs at the same voltage. And due to same issue the current at each branch is same (I_D).

From KVL;

$$I_D = \frac{V_{GS1} - V_{GS2}}{R} = \frac{1}{R} \left(\sqrt{\frac{2I_D}{K_n'(\frac{W}{L})}} + V_{TH} - \sqrt{\frac{2I_D}{K_n' \cdot K (\frac{W}{L})}} - V_{TH} \right)$$

$$I_D = \frac{1}{R} \left(\sqrt{\frac{2I_D}{K_n'(\frac{W}{L})}} \left(1 - \frac{1}{K} \right) \right)$$

$$I_D = \frac{1}{R^2} \frac{2}{K_n'(\frac{W}{L})} \left(1 - \frac{1}{K} \right)^2$$

$$V_{REF} = V_{GS1} = \sqrt{\frac{2I_D}{K_n'(\frac{W}{L})}} + V_{TH} \Rightarrow \boxed{V_{REF} = \frac{2}{K_n'(\frac{W}{L})R} \left(1 - \frac{1}{K} \right) + V_{TH}}$$

\Rightarrow Let's drive the TCF of the circuit.

$$TCV_{REF} = \frac{1}{V_{REF}} \frac{\partial V_{REF}}{\partial T} \Rightarrow \frac{\partial V_{REF}}{\partial T} = \frac{\partial V_{TH}}{\partial T} + \frac{2}{(W/L)(1-1/K)} \frac{\partial}{\partial T} \left(\frac{1}{K_n' R} \right)$$

$$\boxed{\frac{\partial V_{REF}}{\partial T} = \frac{\partial V_{TH}}{\partial T} - \frac{2}{(W/L)(1-1/K)} \times \frac{1}{R K_n'} \left(\frac{1}{K_n'} \frac{\partial K_n'}{\partial T} + \frac{1}{R} \frac{\partial R}{\partial T} \right)}$$