

EE 414 Supplementary Problems

Problem 1: This problem concerns the CMOS op-amp shown in Fig. 1.

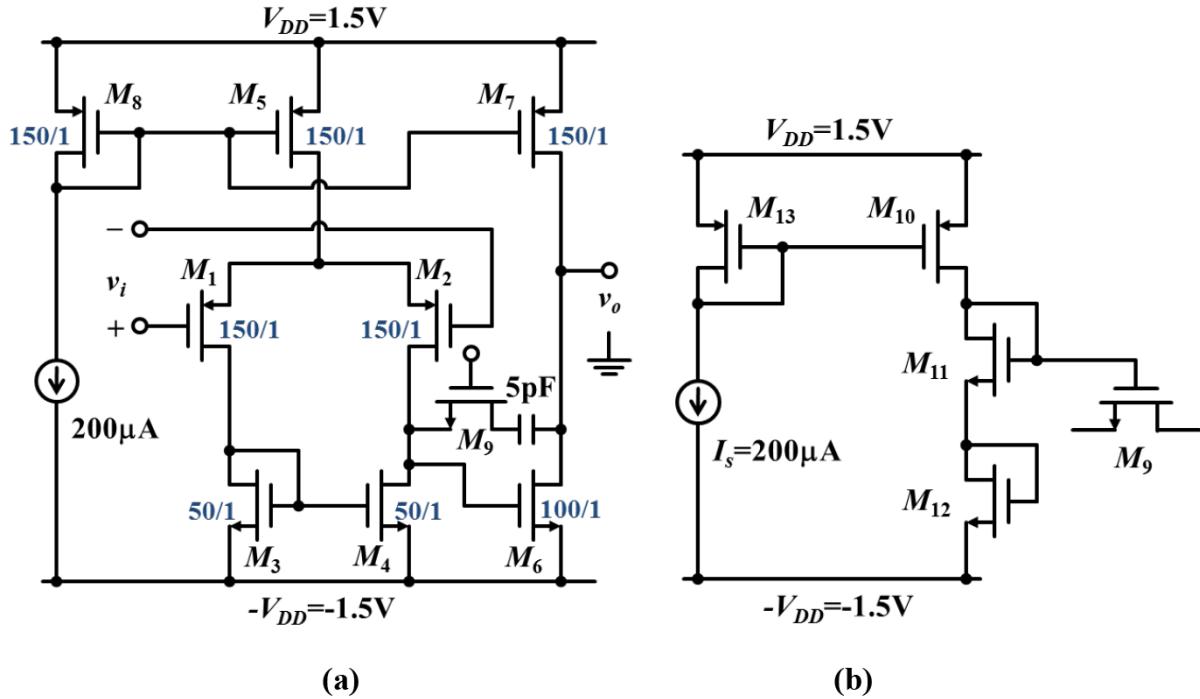


Fig. 1.

Variable	NMOS	PMOS	Unit
X_d	0.1	0.1	μm
dX_d/dV_{ds}	0.02	0.04	$\mu\text{m}/\text{V}$
t_{ox}	80	80	A
μ	450	150	cm^2/Vs
V_t	0.7	0.7	V
γ	0	0	$\text{V}^{-1/2}$

Table 1

- Calculate the open-loop voltage gain, unity-gain bandwidth, and slew rate, for the circuit in Fig. 1 (a). Use the parameters of Table 1. Assume that the gate of M_9 is connected to the positive power supply V_{DD} and that the W/L ratio of M_9 has been chosen to cancel the right half-plane zero.
- If the circuit of Fig. 1 (b) is used to generate the voltage to be applied to the gate of M_9 in Fig. 1 (a), calculate the required W/L ratio of M_9 to move the right-half plane zero to infinity. Let $V_{DD} = 1.5\text{V}$ and $I_s = 200\mu\text{A}$. Use $L = 1\mu\text{m}$ for all transistors, $W_{13} = W_{10} = 150\mu\text{m}$, and $W_{11} = W_{12} = 100\mu\text{m}$. Use Table 1 for other parameters.
- Assuming that the zero has been moved to infinity, determine the maximum load capacitance that can be attached directly to the output node of the circuit in Fig 1 (a) and still maintain a phase margin of 45° . Neglect all higher order poles except the one due to the load capacitance. Use the value of W/L ratio obtained in part (b) for M_9 with the bias circuit of Fig. 1 (b). Ignore junction capacitance for all transistors. Use Table 1 for other parameters.

Problem 2:

What is the gain and -3 dB bandwidth (in Hz) of Fig. 2 if $C_L=1\text{ pF}$? Ignore reverse bias voltage effects on the pn junctions and assume the bulk-source and bulk-drain areas are given by $W \times 5\mu\text{m}$. The W/L ratios for M1 and M2 are $10\mu\text{m}/1\mu\text{m}$ and for the remaining PMOS transistors the W/L ratios are all $2\mu\text{m}/1\mu\text{m}$.

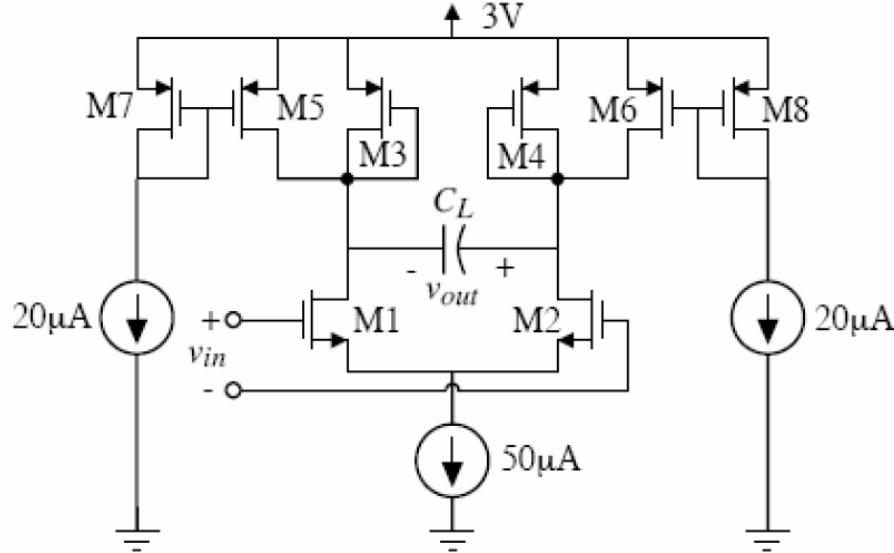


Fig. 2.

Problem 3:

A comparator consists of an amplifier cascaded with a latch as shown below. The amplifier has voltage gain of 10V/V and $f_{-3\text{dB}} = 100\text{MHz}$ and the latch has a time constant of 10ns . The maximum and minimum voltage swings of the amplifier and latch are V_{OH} and V_{OL} . When should the latch be enabled after the application of a step input to the amplifier of $0.05(V_{OH}-V_{OL})$ to get minimum overall propagation time delay? What is the value of the minimum propagation time delay? It may be useful to recall that the propagation time delay of the latch is given as $t_p = \tau_L \ln\left(\frac{V_{OH}-V_{OL}}{2v_{il}}\right)$ where v_{il} is the latch input ($v_{il} = x \cdot (V_{OH} - V_{OL})$).

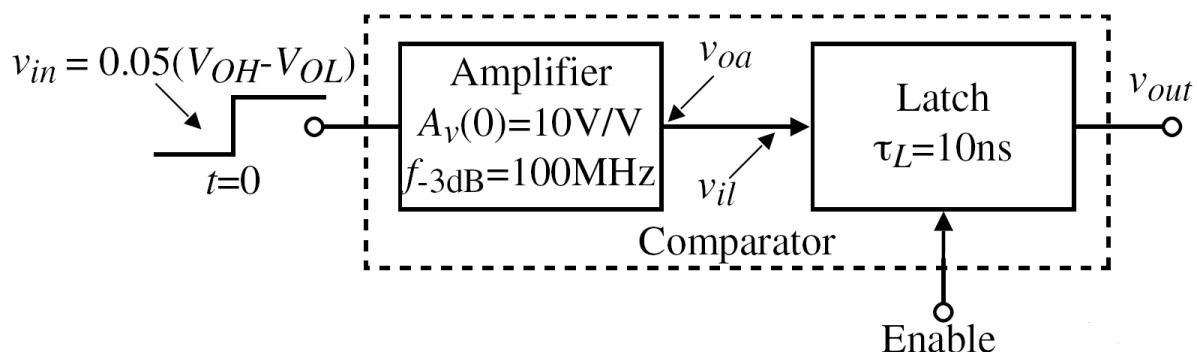


Fig. 3

EE414 Supplementary Problems Solutions

Problem 1:

For $L_d = 0$

$$(a) L_{eff} = L - 2L_d - X_d = 0.9 \mu m$$

$$|I_D| = 200 \mu A \text{ for } M_5 - M_8$$

$$|I_D| = 100 \mu A \text{ for } M_1 - M_4$$

$$\frac{dX_d}{dV_{DS}} = 0.02 \mu m/V \text{ (NMOS)} \\ = 0.04 \mu m/V \text{ (PMOS)}$$

$$\gamma_{f_0} = \frac{\partial I_D}{\partial V_{DS}} = \frac{I_D}{L_{eff}} \frac{dX_d}{dV_{DS}}$$

$$\gamma_{f_02} = \frac{100 \mu A}{0.9 \mu m} \cdot 0.04 \mu m/V = 4.44 \mu A/V$$

$$\gamma_{f_04} = \frac{100 \mu A}{0.9 \mu m} \cdot 0.02 \mu m/V = 2.22 \mu A/V$$

$$C_{ox} = \frac{\epsilon_{ox}}{t_{ox}} = 3.9 \times 8.854 \times 10^{-12} / 80 \times 10^{-10} = 4.32 \times 10^{-3} F/m^2$$

$$K_p' = M_p C_{ox} = 150 \times 10^{-4} \times 4.32 \times 10^{-3} = 64.7 \mu A/V^2$$

$$K_n' = M_n C_{ox} = 450 \times 10^{-4} \times 4.32 \times 10^{-3} = 194 \mu A/V^2$$


$$g_{M_2} = \sqrt{2 \times 64.7 \times (150/0.9) \times 100} = 1.47 \mu A/V$$

$$g_{M_8} = \sqrt{2 \times 194 \times (100/0.9) \times 200} = 2.94 \mu A/V$$

$$\gamma_{f_07} = \frac{200 \mu A}{0.9 \mu m} \times 0.04 \mu m/V = 8.89 \mu A/V$$

$$\gamma_{f_06} = \frac{200 \mu A}{0.9 \mu m} \times 0.02 \mu m/V = 4.44 \mu A/V$$
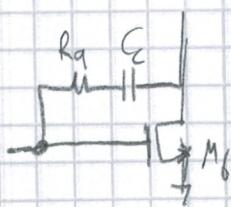
$$V_o/V_i = g_{M_2} (\gamma_{f_02}/\gamma_{f_04}) \cdot g_{M_6} (\gamma_{f_06}/\gamma_{f_07}) = \underline{4.8681}$$



$$Z = \frac{1}{(\gamma_{g_{M_6}} - R_g) C_L}$$

Cancel this zero by moving it to infinity.

$$R_g = \frac{1}{g_m} = \frac{1}{2.94 \text{ m}} = 340.1 \Omega$$

$$\gamma R_g = K' \left(\frac{w}{L} \right)_q (V_{GSq} - V_{Tq} - V_{DSq}) \Rightarrow (V_{DSq} \approx 0)$$

Assume $\gamma = 0$

$$\gamma R_g = K' \left(\frac{w}{L} \right)_q (V_{GSq} - V_{SS} - V_{GSG} - V_{Tq})$$

$$\therefore V_{DSq} = \sqrt{\frac{2 \times 700}{194 \times 100 \times 0.9}} = 0.136 \text{ V} \Rightarrow V_{GSq} = V_{DSq} + V_{TF} = 0.136 \text{ V} + 0.6 \text{ V}$$

$$\therefore \gamma R_g = \frac{1}{340} = 194 \times 10^6 \left(\frac{w}{L} \right)_q (0.136 - 0.7) \Rightarrow \left(\frac{w}{L} \right)_q = 9.7$$

* M_q is in triode region, so $X_d = 0 \Rightarrow L_q = L_d - 2L_s - X_d = 1 \text{ mm}$

$$\Rightarrow L_q = 1 \text{ mm}, W_q = 9.7 \text{ mm}$$

$$\text{At funity} \Rightarrow |A(j\omega)| = \left| \frac{g_m}{j\omega C_c} \right| = 1 \Rightarrow \text{funity} = \frac{g_m}{C_c 2\pi} = 46.8 \text{ MHz}$$

$$SR = \frac{I_{max}}{C_c} = \frac{200 \mu A}{5 \text{ pF}} = 40 \text{ V/}\mu\text{s}$$

$$(b) \gamma R_g = K' \left(\frac{w}{L} \right)_q (V_{GSq} - V_{Tq})$$

$$\text{Since } I_{D12} = I_{D6} \text{ and } \left(\frac{w}{L} \right)_{12} = \left(\frac{w}{L} \right)_6 \therefore V_{DS12} = V_{DS6} = 0.136 \text{ V}$$

$$\text{Therefore } V_{SS11} = V_{SS12} = V_{T12} + V_{DS12} = V_{SSq} = V_{GSG} = V_{T6} + V_{DS6}$$

Because $V_{T12} = V_{T6}$ (no body effect)

$$\text{Also: } V_{DS11} = V_{DS12} \text{ because } I_{D11} = I_{D12} \text{ and } \left(\frac{w}{L} \right)_{11} = \left(\frac{w}{L} \right)_{12}$$

$$\begin{aligned} \text{Therefore: } V_{GSq} &= V_{GS11} + V_{GS12} - V_{GSG} = V_{G11} + V_{DS11} + V_{G12} + V_{DS12} - V_{G6} - V_{DS6} \\ &= V_{G11} + V_{DS11} \end{aligned}$$

$$\therefore V_{GSq} - V_{Tq} = V_{T11} + V_{oV11} - V_{Tq} = V_{oV11}$$

Since $V_{GSq} - V_{Tq} = V_{GS6} - V_{T6}$ and γ_{Rq} should be equal to g_{m6} to cancel the RHP zero.

$$\gamma_{Rq} = k'(w_L)q(V_{GSq} - V_{Tq}) = g_{m6} = k'(w_L)(V_{GS6} - V_{T6})$$

$$\Rightarrow (w_L)q = (w_L)_6 = \underline{\underline{100/1}}$$

(c) To get 45° phase margin set the second pole = unity gain freq.

$$(|P_2| = \frac{g_{m6}C_c}{C_L C_c + C_c C_L + C_C c}) = \frac{g_{m2}}{C_c} \quad \begin{matrix} (C_c \text{ is the parasitic cap.}) \\ (\text{at first stage output}) \end{matrix}$$

$$\therefore C_1 = C_{oL2} + C_{oL4} + C_{GS6} + C_{oVq} \approx C_{GS6} = \left(\frac{2}{3} 100\mu m \cdot 0.9\mu m\right) \cdot \frac{632 fF}{\mu m^2}$$

$$C_1 = 259.2 fF$$


$$\frac{g_{m2}}{C_c} = \frac{147 \text{ mA/V}}{5 \text{ pF}} = 294 \text{ Mrad/s}$$

$$\therefore 294 \text{ Mrad/s} = \frac{2.94 \text{ mA/V} \cdot 5 \text{ pF}}{C_L 259.2 fF + C_L 59 + 259.2 fF \times 5 \text{ pF}}$$

$$\Rightarrow C_L = 9.26 \text{ pF}$$

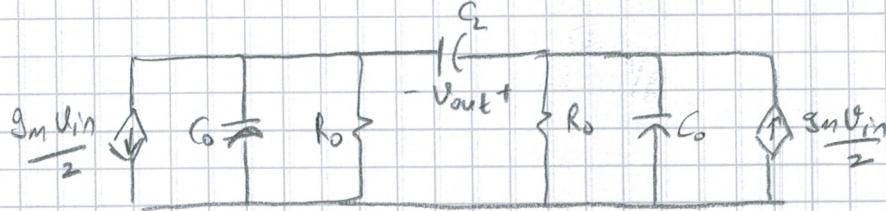Problem 2:

Let's first draw the small signal model of the circuit.



$$\frac{V_{out}}{V_{in}} = g_m R_0 \quad \text{and} \quad \omega_{-3dB} = \frac{1}{(C_L + 2C_0) 2R_0}$$

$$g_m = \sqrt{2 K'_N \left(\frac{W}{L}\right)_1 I_{D1}} = \sqrt{2 \cdot 110 \cdot 10 \cdot 2.5} \text{ mA/V} = 234.5 \text{ mA/V}$$

$$R_0 \approx 1/g_{m3} \parallel r_{o1} \parallel r_{o3} \parallel r_{o5}, \quad g_{m3} = \sqrt{2 K'_P \left(\frac{W}{L}\right)_3 I_{D3}} = \sqrt{2 \cdot 50 \cdot 2.5} \text{ mA/V} = 31.62 \text{ mA/V}$$

$$r_{o1} = \frac{1}{2I_{D1}} = \frac{1}{0.04 \times 2.5 \text{ mA}} = 1 \text{ M}\Omega, \quad r_{o3} = 4 \text{ M}\Omega, \quad r_{o5} = 0.8 \text{ M}\Omega$$

$$\therefore R_0 = 31.623 \text{ k}\Omega \parallel 1 \text{ M}\Omega \parallel 4 \text{ M}\Omega \parallel 0.8 \text{ M}\Omega = 29.31 \text{ k}\Omega$$

$$C_0 \approx C_{GS3} + C_{BS1} + C_{BD3} + C_{BD5} \quad C_{GS3} = C_{GS0} W_S + 0.67 C_{ox} W_S L_S \\ = 220 \text{ pF/m} \cdot 2 \times 10^6 + 0.67 \times 26.7 \times 10^{-12} \text{ F/m}^2 \times 2 \mu\text{m}^2$$

$$C_{GS3} = 3.73 \text{ fF}$$

$$C_{BD1} = C_J AS + C_{JSW} \cdot P_S = 770 \times 10^6 \text{ pF/m}^2 \cdot 50 \mu\text{m}^2 + 380 \times 10^{12} \text{ F/m} \cdot 30 \mu\text{m}$$

$$C_{BD1} = 38.5 \text{ pF} + 11.4 \text{ pF} = 49.9 \text{ pF}$$

$$C_{BD3} = C_{BD5} = 560 \times 10^6 \text{ pF/m}^2 \cdot 10 \mu\text{m}^2 + 350 \times 10^{12} \text{ F/m} \cdot 14 \mu\text{m} = 10.5 \text{ pF}$$


$$\therefore C_0 = 74.6 \text{ fF} \rightarrow \omega_{-3dB} = \frac{1}{(110.73 \text{ pF}) 58.62 \text{ k}\Omega} = 16.65 \text{ rad/s}$$

$$\underline{\underline{f_{-3dB} = 2.62 \text{ MHz}}}$$

$$\underline{\underline{A_V = 6.873 \text{ V/V}}}$$

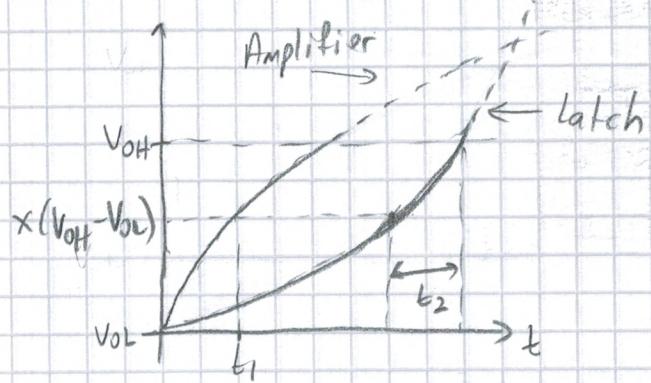Problem 3 i

The solution is based on the figure shown.



Note that $V_{oa}(t) = 10 [1 - e^{-\frac{\omega_{3dB}}{2} t}] \cdot 0.05 (V_{OH} - V_{OL})$

If we define the input voltage to the latch as,

$$V_{ip} = x(V_{OH} - V_{OL}) \text{ then we can solve for } t_1 \text{ & } t_2 \text{ as:}$$

$$x(V_{OH} - V_{OL}) = 10 [1 - e^{-\frac{\omega_{3dB}}{2} t}] \cdot 0.05 (V_{OH} - V_{OL})$$

$$\hookrightarrow x = 0.5 [1 - e^{-\frac{\omega_{3dB}}{2} t}]$$

This gives,

$$t_1 = \frac{1}{\omega_{3dB}} \ln \left(\frac{1}{1-2x} \right)$$

From the propagation time delay of the latch we get,

$$t_2 = \tau_L \ln \left(\frac{V_{OH} - V_{OL}}{2V_{ip}} \right) = \tau_L \ln \left(\frac{1}{2x} \right)$$

$$\therefore t_p = t_1 + t_2 = \frac{1}{\omega_{3dB}} \ln \left(\frac{1}{1-2x} \right) + \tau_L \ln \left(\frac{1}{2x} \right)$$

$$\frac{dt_p}{dx} = 0 \text{ gives } x = \frac{1}{1+2\pi} = 0.4313 \quad t_1 = \frac{10ns}{2\pi} \ln(1+2\pi) = \underline{\underline{3.16ns}}$$

$$t_2 = 10ns \ln \left(\frac{1+2\pi}{2\pi} \right) = \underline{\underline{1.477 ns}}$$