
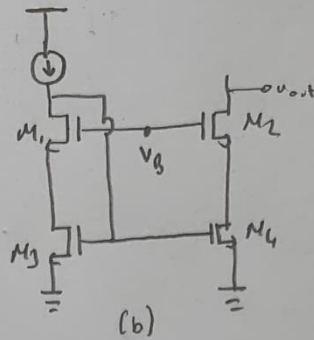


THE-I Solutions

1.

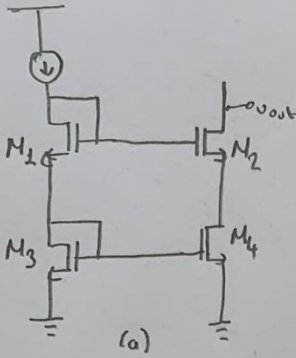

$$R_{out(a)} = R_{out(b)} = r_{o4} + r_{o2} + g_{m2} r_{o2} r_{o4}$$

$$V_{out(a)} \geq 2V_{GS} - V_{TN} \Rightarrow V_{out(a)min} = 2V_{GS} - V_{TN}$$

$$V_{out(b)} \geq V_b - V_{TN}$$


$$2V_{GS} - V_{TN} \leq V_b \leq V_{TN} + V_{GS}$$

To obtain max swing V_{outmin} must be minimized.

$$V_{out(b)min} = 2V_{GS} - 2V_{TN}$$

- Both have same output resistance
- Modified version has larger swing (V_{TN})
- Modified version requires external biasing.

2.

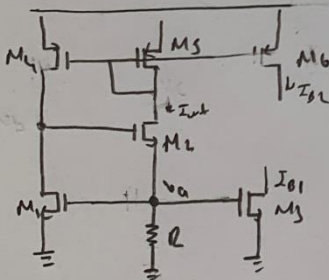

$$v_a = v_{out} + V_{TN}$$

$$k_n = \mu_n \cdot \frac{W}{L} \cdot C_{ox}$$

$$k_p = \mu_p \cdot \frac{W}{L} \cdot C_{ox}$$

$$\left. \begin{aligned} I_{D1} &= \frac{1}{2} k_{n1} v_{a1}^2 \\ I_{D4} &= \frac{1}{2} k_{p4} v_{a4}^2 \\ I_{int} &= \frac{1}{2} k_{p5} v_{a5}^2 \end{aligned} \right\} \begin{aligned} I_{D1} &= I_{D4} \\ I_{D4} &= \frac{k_{p5}}{k_{p4}} I_{int} \end{aligned} \Rightarrow v_{a5} = \sqrt{\frac{2 I_{int} \cdot k_{p4}}{k_{n1} \cdot k_{p5}}}$$

$$v_a = v_{a1} + V_{TN} = I_{int} R$$

$$I_{int} = \left(\sqrt{\frac{2 I_{int} \cdot k_{p4}}{k_{n1} \cdot k_{p5}}} + V_{TN} \right) \cdot \frac{1}{R}$$

$$I_{int} = \left(\frac{\sqrt{\frac{2 k_{p4}}{k_{n1} k_{p5}}} + \sqrt{\frac{2 k_{p4}}{k_{n1} k_{p5}} + 4 R V_{TN}}}{2 R} \right)^2$$

$$I_{D3} = I_{D1} = \frac{k_{n3}}{k_{n1}} I_{D1} = \frac{k_{n3}}{k_{n1}} \cdot \frac{k_{p4}}{k_{p5}} I_{int}$$

$$I_{D1} = \frac{k_{n3} \cdot k_{p4}}{k_{n1} \cdot k_{p5}} \cdot \left(\frac{\sqrt{\frac{2 k_{p4}}{k_{n1} k_{p5}}} + \sqrt{\frac{2 k_{p4}}{k_{n1} k_{p5}} + 4 R V_{TN}}}{2 R} \right)^2$$

$$I_{D6} = I_{D2} = \frac{k_{p6}}{k_{p5}} \cdot I_{int}$$

$$I_{D2} = \frac{k_{p6}}{k_{p5}} \cdot \left(\frac{\sqrt{\frac{2 k_{p4}}{k_{n1} k_{p5}}} + \sqrt{\frac{2 k_{p4}}{k_{n1} k_{p5}} + 4 R V_{TN}}}{2 R} \right)^2$$